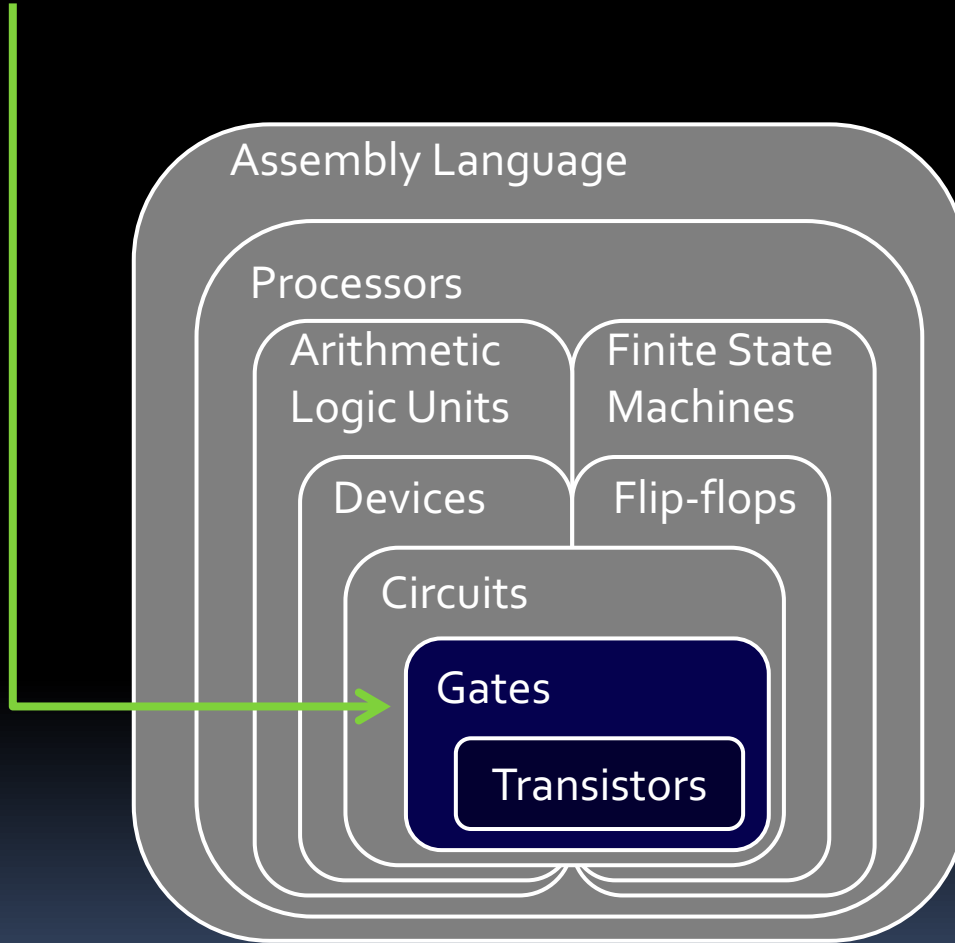




# Week 2: Circuit Creation

# You are here



 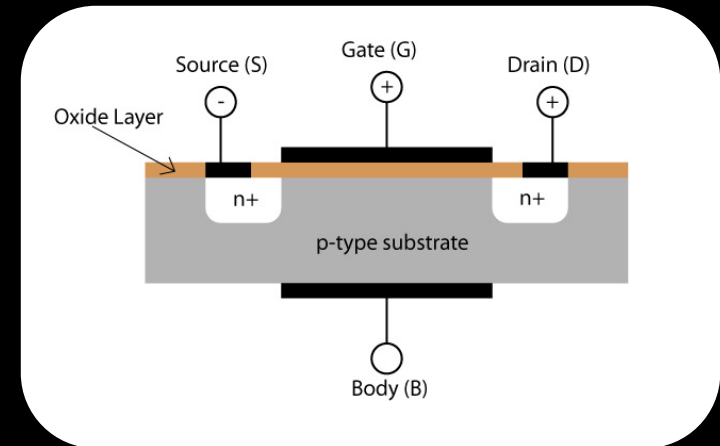
# From transistors to gates

- Transistors are semiconductor circuits that can connect the **source** and the **drain** together, depending on the voltage value at the **gate**.
  - **NPN** transistors (**nMOS**) are connected when the gate value is high.
  - **PNP** transistors (**pMOS**) are connected when the gate value is low.
- These are then used to make **digital logic gates**.




# Transistor notation


- NPN transistor:

 

- PNP transistor:

 


- Voltage values:

 



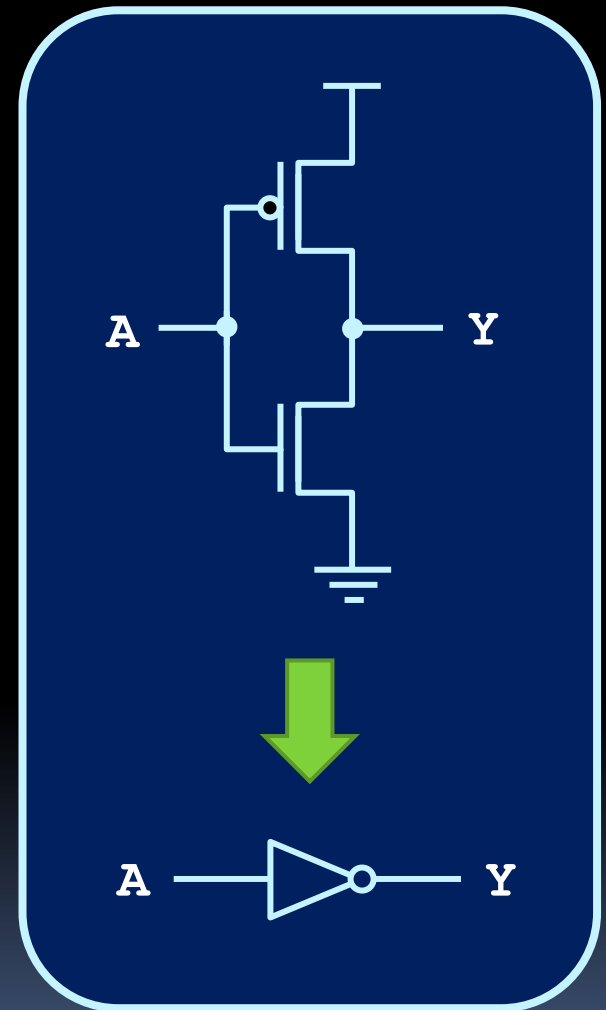
# How gates are made

- To create logic gates:
  - Remember that transistors act like faucets for electricity.
  - The inputs to the logic gates determine if the outputs will be connected to high or low voltage.
  - Example: NOT gates:



# Creating circuits with gates

 

# Making logic with gates


- Logic gates like the following allow us to create an output value, based on one or more input values.
  - Each corresponds to Boolean logic that we've seen before in CSCAo8/A48/A67:



A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1



A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

 

A	Y
0	1
1	0

# Aside: notation


- While we're talking about notation...
  - **AND** operations are denoted in these expressions by the multiplication symbol.
    - e.g.  $A \cdot B \cdot C$  or  $A * B * C \approx A \wedge B \wedge C$
  - **OR** operations are denoted by the addition symbol.
    - e.g.  $A + B + C \approx A \vee B \vee C$
  - NOT is denoted by multiple symbols.
    - e.g.  $\neg A$  or  $A'$  or  $\bar{A}$
  - **XOR** occurs rarely in circuit expressions.
    - e.g.  $A \oplus B$

# Making boolean expressions


- So how would you represent boolean expressions using logic gates?

$$Y = (A \text{ or } B) \text{ and } (\text{not } A \text{ or } \text{not } B) \text{ or } C$$

- Like so:

 


# Now you are here

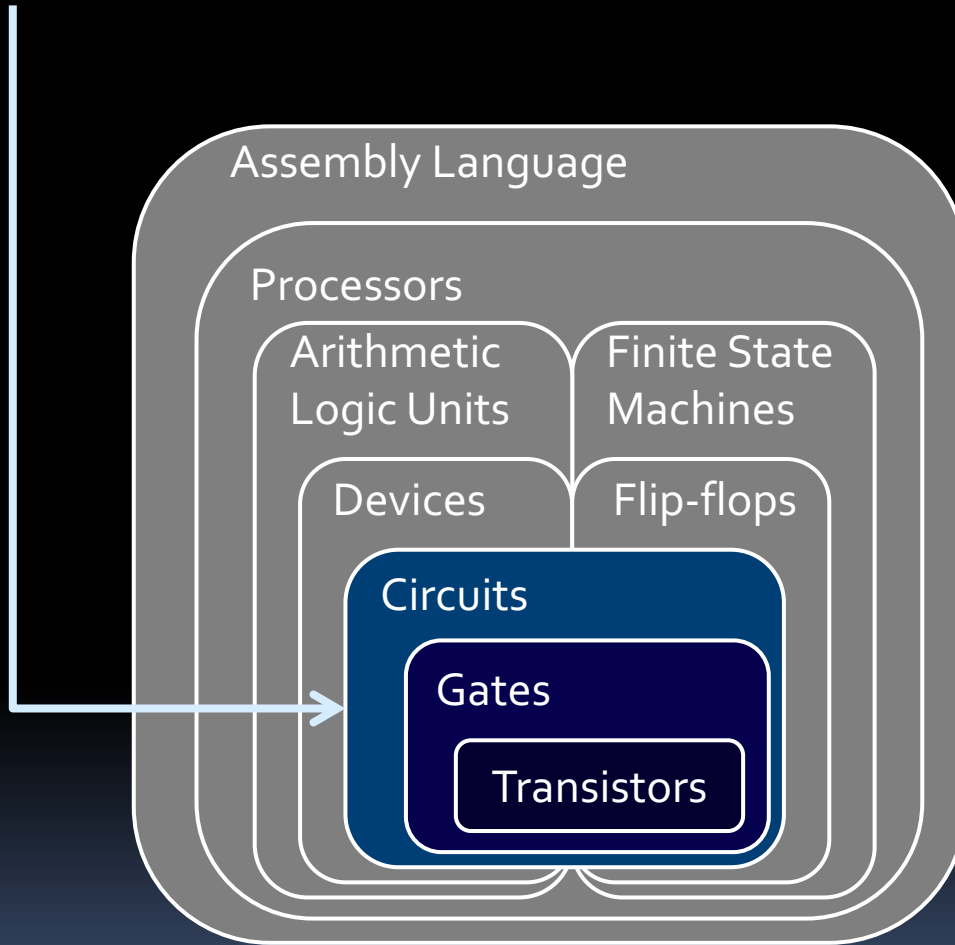

 
# Creating complex circuits

- What do we do in the case of more complex circuits, with several inputs and more than one output?
  - If you're lucky, a truth table is provided to express the circuit.
  - Usually the behaviour of the circuit is expressed in words, and the first step involves creating a truth table that represents the described behaviour.


 
# Circuit example

- The circuit on the right has three inputs (A, B and C) and two outputs (X and Y).



- What logic is needed to set X high when all three inputs are high?
- What logic is needed to set Y high when the number of high inputs is odd?



# Combinational circuits


- Small problems can be solved easily.



- Larger problems require a more systematic approach.
  - Example: Given three inputs A, B, and C, make output Y high in the case where all of the inputs are low, or when A and B are low and C is high, or when A and C are low but B is high, or when A is low and B and C are high.
 
# Creating complex logic

- How do we approach problems like these (and circuit problems in general)?
- **Basic steps:**
  1. Create truth tables.
  2. Express as boolean expression.
  3. Convert to gates.
- The key to an efficient design?
  - Spending extra time on Step #2.




# Example truth table

- Consider the following example:
  - *"Given three inputs  $A$ ,  $B$ , and  $C$ , make output  $Y$  high wherever any of the inputs are low, except when all three are low or when  $A$  and  $C$  are high."*
  - This leads to the truth table on the right.
  - Is there a more compact way to describe this?

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0


# Minterms and Maxterms

 

# Minterms

- An easier way to express circuit behaviour is to assume the **standard truth table format**, and then list which input rows cause **high output**.
  - These rows are referred to as **minterms**.

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

 

Minterm	Y
$m_0$	0
$m_1$	1
$m_2$	1
$m_3$	1
$m_4$	1
$m_5$	0
$m_6$	1
$m_7$	0

# Minterms and maxterms

- A more formal description:
  - **Minterm** = an AND expression with every input present in true or complemented form.
  - **Maxterm** = an OR expression with every input present in true or complemented form.
  - For example, given four inputs (A, B, C, D):
    - Valid minterms:
      - $A \cdot \bar{B} \cdot C \cdot D, \bar{A} \cdot B \cdot \bar{C} \cdot D, A \cdot B \cdot C \cdot D$
    - Valid maxterms:
      - $A + \bar{B} + C + D, \bar{A} + B + \bar{C} + D, A + B + C + D$
    - Neither minterm nor maxterm:
      - $A \cdot B + C \cdot D, A \cdot B \cdot D, A + B$

# What is This For?

- Minterms and maxterms are a shorthand to refer to **rows of the truth table**.
- **minterms** describe rows where output is **high**.
- **maxterms** describe rows where output is **low**.
- We then OR minterms or AND maxterms.
  - Don't mix them both

# Back to minterms

- Circuits are often described using minterms or maxterms, as a form of logic shorthand.
  - Given  $n$  inputs, there are  $2^n$  minterms and maxterms possible (same as rows in a truth table).
  - Naming scheme:
    - **Minterms** are labeled as  $m_x$ , **maxterms** are labeled as  $M_x$ 
      - The  **$x$  subscript** indicates the row in the truth table.
      - $x$  starts at 0, and ends with  $n-1$ .
  - Example: Given 3 inputs –
    - Minterms are  $m_0 (\bar{A} \cdot \bar{B} \cdot \bar{C})$  to  $m_7 (A \cdot B \cdot C)$
    - Maxterms are  $M_0 (A+B+C)$  to  $M_7 (\bar{A}+\bar{B}+\bar{C})$



# Quick Exercises

- Given 4 inputs  $A, B, C$  and  $D$  write:

- $m_9$

- $m_{15}$

- $m_{16}$

- $M_2$



- Which minterm is this?

- $\bar{A} \cdot B \cdot \bar{C} \cdot \bar{D}$



- Which maxterm is this?

- $A+B+C+\bar{D}$



# $m_0$ vs $M_0$

- $m_0$  is  $\bar{A}$  and  $\bar{B}$  and  $\bar{C}$ 
  - $m_0 = 1$  iff  $A = B = C = 0$  (row 0)
- $M_0$  is  $A$  or  $B$  or  $C$ 
  - $M_0 = 0$  iff  $A = B = C = 0$  (row 0)
- **Minterms tell us when the output is 1**
- **Maxterms tell us when the input is 0**

# Using minterms and maxterms

- What are minterms used for?
  - A single minterm indicates a set of inputs that will make the output go high.
  - Example:  $m_2$
  - Output **only goes high in third row** of truth table.

A	B	C	D	$m_2$
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

# Using minterms and maxterms

- What happens when you **OR** two **minterms**?
  - Result is output that goes high in both minterm cases.
  - For  $m_2+m_8$ , both third and ninth rows of truth table result in high output.

A	B	C	D	$m_2$	$m_8$	$m_2+m_8$
0	0	0	0	0	0	
0	0	0	1	0	0	
0	0	1	0	1	0	
0	0	1	1	0	0	
0	1	0	0	0	0	
0	1	0	1	0	0	
0	1	1	0	0	0	
0	1	1	1	0	0	
1	0	0	0	0	1	
1	0	0	1	0	0	
1	0	1	0	0	0	
1	0	1	1	0	0	
1	1	0	0	0	0	
1	1	0	1	0	0	
1	1	1	0	0	0	
1	1	1	1	0	0	

# Creating Boolean expressions

- Two canonical forms of Boolean expressions:
  - **Sum-of-Minterms (SOM):**
    - Since each minterm corresponds to a single high output in the truth table, the combined high outputs are a **union** of these minterm expressions.
    - Also known as: Sum-of-Products.
  - **Product-of-Maxterms (POM):**
    - Since each maxterm only produces a single low output in the truth table, the combined low outputs are an **intersection** of these maxterm expressions.
    - Also known as Product-of-Sums.

$$Y = m_2 + m_6 + m_7 + m_{10} \quad (\text{SOM})$$

A	B	C	D	$m_2$	$m_6$	$m_7$	$m_{10}$	Y
0	0	0	0					
0	0	0	1					
0	0	1	0					
0	0	1	1					
0	1	0	0					
0	1	0	1					
0	1	1	0					
0	1	1	1					
1	0	0	0					
1	0	0	1					
1	0	1	0					
1	0	1	1					
1	1	0	0					
1	1	0	1					
1	1	1	0					
1	1	1	1					

$$Y = M_3 \cdot M_5 \cdot M_7 \cdot M_{10} \cdot M_{14} \quad (\text{POM})$$

A	B	C	D	M <sub>3</sub>	M <sub>5</sub>	M <sub>7</sub>	M <sub>10</sub>	M <sub>14</sub>	Y
0	0	0	0						
0	0	0	1						
0	0	1	0						
0	0	1	1						
0	1	0	0						
0	1	0	1						
0	1	1	0						
0	1	1	1						
1	0	0	0						
1	0	0	1						
1	0	1	0						
1	0	1	1						
1	1	0	0						
1	1	0	1						
1	1	1	0						
1	1	1	1						

# Using Sum-of-Minterms

- Sum-of-Minterms is a way of expressing which inputs cause the output to go high. Product-of-Maxterms is a way of expression which inputs cause the output to go low.
  - Assumes that the truth table columns list the inputs according to some logical or natural order.
- Minterm and maxterm expressions are used for efficiency reasons:
  - More compact than displaying entire truth tables.
  - Sum-of-minterms are useful in cases with very few input combinations that produce high output.
    - Product-of-maxterms useful when expressing truth tables that have very few low output cases...




# Converting SOM to gates


- Once you have a Sum-of-Minterms expression, it is easy to convert this to the equivalent combination of gates:

$$m_0 + m_1 + m_2 + m_3 =$$

 
$$\bar{A} \cdot \bar{B} \cdot \bar{C} + \bar{A} \cdot \bar{B} \cdot C + \bar{A} \cdot B \cdot \bar{C} + \bar{A} \cdot B \cdot C =$$



# Break

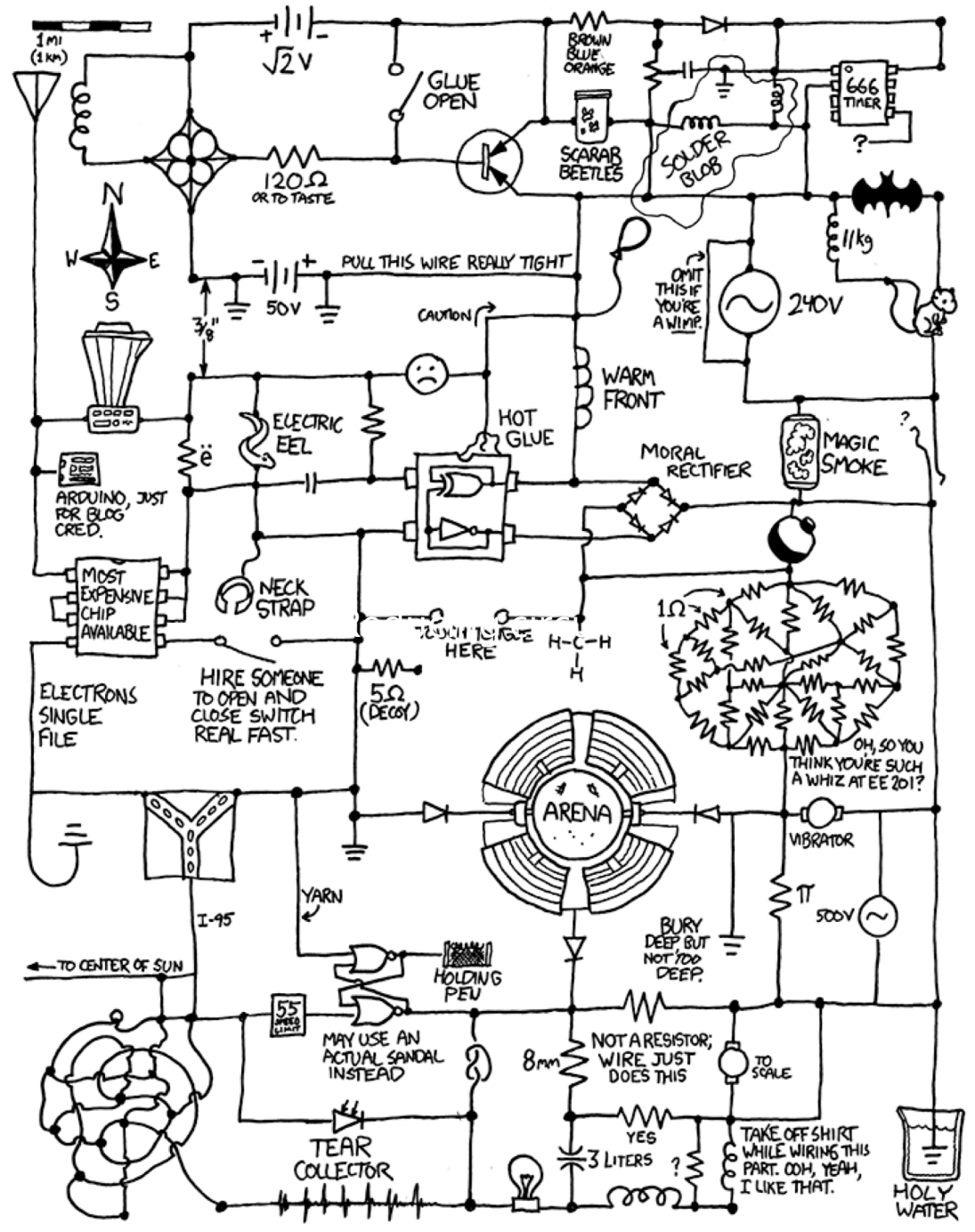


# Reducing circuits

 


# Which is Better?

- Which implementation do you prefer? Why?


A.

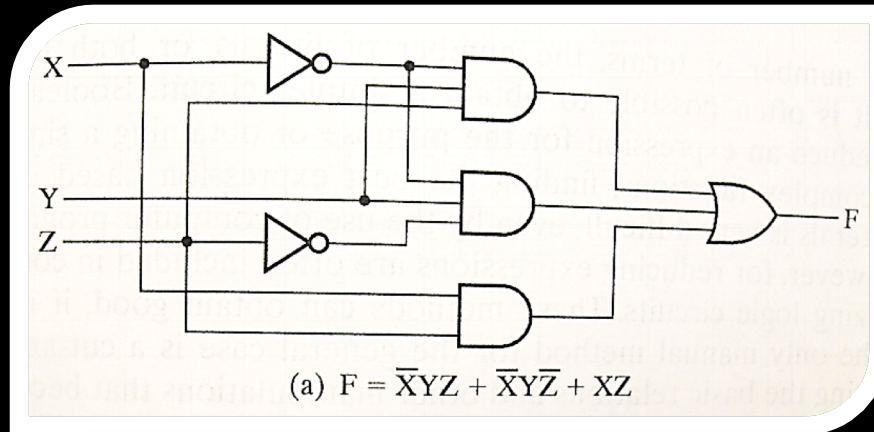

B.

 

# Reasons for reducing circuits

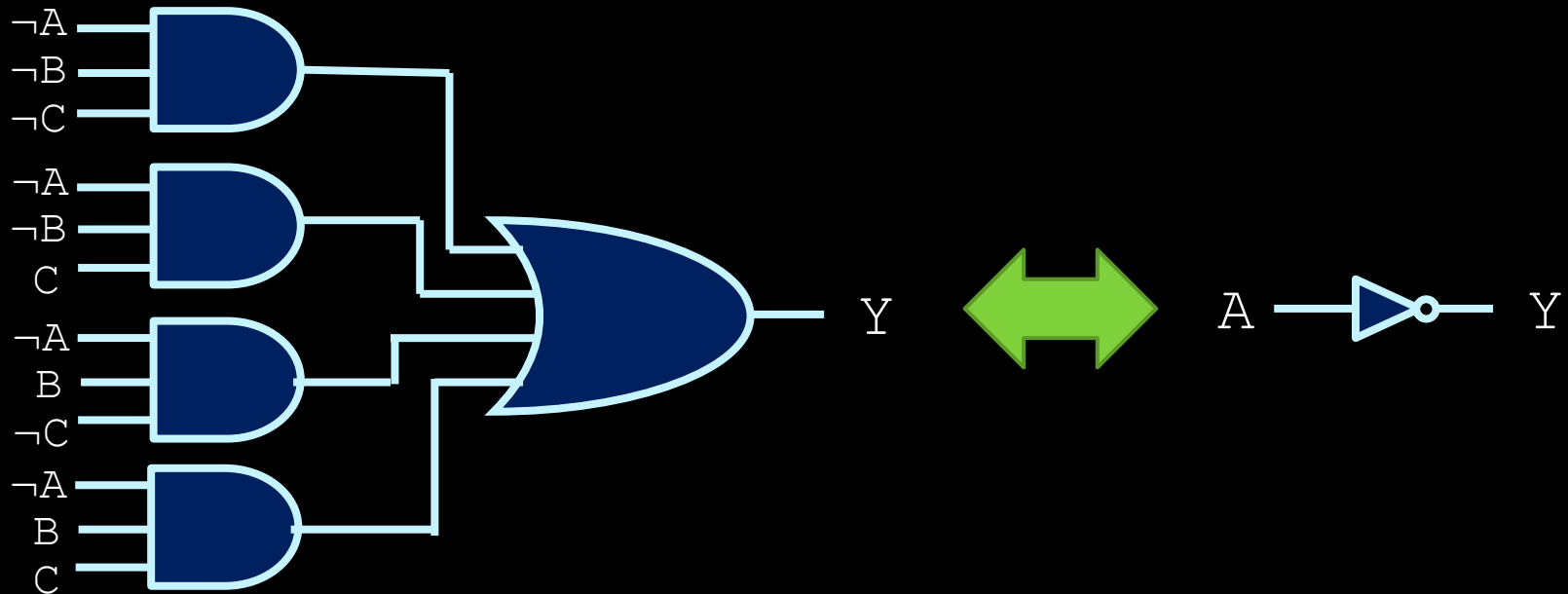

- Note example of Sum-of-Minterms circuit design.
- To minimize the number of gates, we want to reduce the boolean expression as much as possible from a collection of minterms to something smaller.
- This is where CSCA67 skills come in handy 😊

# Boolean algebra review

- Axioms:

$$\begin{array}{ll} 0 \cdot 0 = 0 & 0 \cdot 1 = 1 \cdot 0 = 0 \\ 1 \cdot 1 = 1 & \text{if } x = 1, \bar{x} = 0 \end{array}$$

- From this, we can extrapolate:

If one input of a 2-input AND gate is 1, then the output is whatever value the other input is.

$$\begin{array}{ll} x \cdot 0 = & x + 1 = \\ x \cdot 1 = & x + 0 = \\ x \cdot x = & x + x = \\ x \cdot \bar{x} = & x + \bar{x} = \\ \bar{\bar{x}} = & \end{array}$$

If one input of a 2-input OR gate is 0, then the output is whatever value the other input is.

# Other Boolean identities

- Commutative Law:

$$x \cdot y = y \cdot x \qquad x + y = y + x$$

- Associative Law:

$$x \cdot (y \cdot z) = (x \cdot y) \cdot z$$
$$x + (y + z) = (x + y) + z$$

- Distributive Law:

$$x \cdot (y + z) = x \cdot y + x \cdot z$$
$$x + (y \cdot z) = (x + y) \cdot (x + z)$$

Does this hold in conventional algebra?

# Other boolean identities


- Simplification Law:

$$x + (\bar{x} \cdot y) = x + y \qquad x \cdot (\bar{x} + y) = x \cdot y$$

- Consensus Law:

$$x \cdot y + \bar{x} \cdot z + y \cdot z = x \cdot y + \bar{x} \cdot z$$

- Proof by Venn diagram:

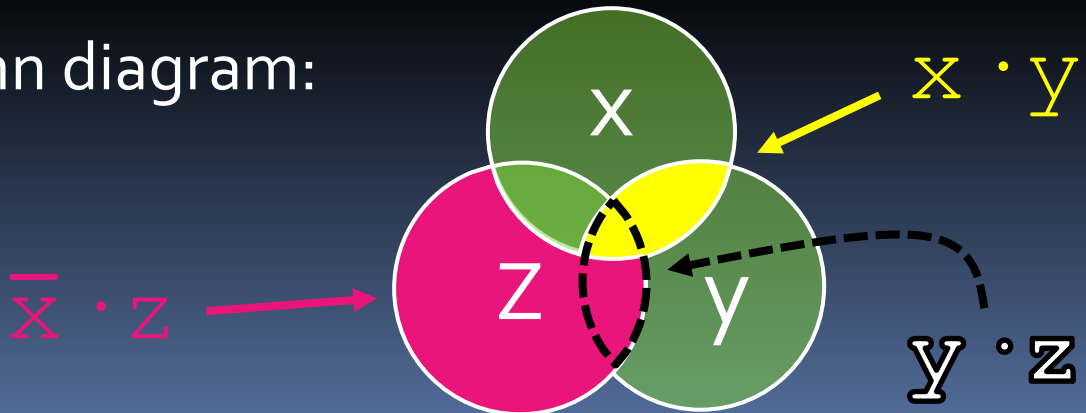



# Other boolean identities

- Absorption Law:

$$x \cdot (x+y) = x$$

$$x + (x \cdot y) = x$$

- De Morgan's Laws:


$$\overline{x \cdot y} = \overline{x} + \overline{y}$$

$$\overline{x + y} = \overline{x} \cdot \overline{y}$$



 
# Converting to NAND gates

- De Morgan's Law is important because out of all the gates, NANDs are the cheapest to fabricate.
  - a Sum-of-Products circuit could be converted into an equivalent circuit of NAND gates:



- This is all based on de Morgan's Law:

 

# Reducing boolean expressions

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

- Using SOM:

$$Y = \bar{A} \cdot B \cdot C + A \cdot \bar{B} \cdot \bar{C} + \boxed{A \cdot B \cdot \bar{C}} + \boxed{A \cdot B \cdot C}$$

- Now start combining terms, like the last two:

$$Y = \bar{A} \cdot B \cdot C + A \cdot \bar{B} \cdot \bar{C} + \boxed{A \cdot B}$$

# Reducing Boolean expressions

- Different final expressions possible, depending on what terms you combine.
- For instance, given the previous example:

$$Y = \bar{A} \cdot B \cdot C + A \cdot \bar{B} \cdot \bar{C} + A \cdot B \cdot \bar{C} + A \cdot B \cdot C$$


- If you combine the end and middle terms...

$$Y = B \cdot C + A \cdot \bar{C}$$

- Which reduces the number of gates and inputs!
 
# Reducing Boolean expressions

- What is considered the “simplest” expression?
  - In this case, “simple” denotes the lowest **gate cost** (G) or the lowest **gate cost with NOTs** (GN).
  - To calculate the gate cost, simply add all the gates together (as well as the cost of the NOT gates, in the case of the GN cost).
  - In this example the cost per gate is 1



# Karnaugh maps

0	0	1	1
0	0	1	1
0	0	0	1
0	1	1	1

# Reducing Boolean expressions

- How do we find the “simplest” expression for a circuit?
  - Technique called **Karnaugh maps** (or K-maps).
  - Karnaugh maps are a 2D grid of minterms, where adjacent minterm locations in the grid differ by a single literal.
  - Values of the grid are the output for that minterm.

	$\bar{B} \cdot \bar{C}$	$\bar{B} \cdot C$	$B \cdot C$	$B \cdot \bar{C}$
$\bar{A}$	0	0	1	0
A	1	0	1	1

# Karnaugh maps

- Karnaugh maps can be of any size, and have any number of inputs.
  - 4 inputs here

	$\bar{C} \cdot \bar{D}$	$\bar{C} \cdot D$	$C \cdot D$	$C \cdot \bar{D}$
$\bar{A} \cdot \bar{B}$	$m_0$	$m_1$	$m_3$	$m_2$
$\bar{A} \cdot B$	$m_4$	$m_5$	$m_7$	$m_6$
$A \cdot B$	$m_{12}$	$m_{13}$	$m_{15}$	$m_{14}$
$A \cdot \bar{B}$	$m_8$	$m_9$	$m_{11}$	$m_{10}$

- Since adjacent minterms only differ by a single value, they can be grouped into a single term that omits that value.



# Using Karnaugh maps


- Once Karnaugh maps are created, draw boxes over groups of high output values.
  - Boxes must be **rectangular, and aligned** with map.
  - Number of values contained within each box must be a **power of 2**.
  - Boxes **may overlap** with each other.
  - Boxes **may wrap across edges of map**.

	$\bar{B} \cdot \bar{C}$	$\bar{B} \cdot C$	$B \cdot C$	$B \cdot \bar{C}$
$\bar{A}$	0	0	1	0
$A$	1	0	1	1

# Using Karnaugh maps

	$\bar{B} \cdot \bar{C}$	$\bar{B} \cdot C$	$B \cdot C$	$B \cdot \bar{C}$
$\bar{A}$	0	0	1	0
$A$	1	0	1	1

 - Once you find the minimal number of boxes that cover all the high outputs, create Boolean expressions from the inputs that are common to all elements in the box.
- For this example:
  - Vertical box:  $B \cdot C$
  - Horizontal box:  $A \cdot \bar{C}$
  - Overall equation:  $Y = B \cdot C + A \cdot \bar{C}$



# Karnaugh maps and maxterms

- Can also use this technique to group maxterms together as well.

- Karnaugh maps with **maxterms** involves grouping

**the zero entries** together, instead of grouping the entries with one values.

	$C+D$	$C+\bar{D}$	$\bar{C}+\bar{D}$	$\bar{C}+D$
$A+B$	$M_0$	$M_1$	$M_3$	$M_2$
$A+\bar{B}$	$M_4$	$M_5$	$M_7$	$M_6$
$\bar{A}+\bar{B}$	$M_{12}$	$M_{13}$	$M_{15}$	$M_{14}$
$\bar{A}+B$	$M_8$	$M_9$	$M_{11}$	$M_{10}$

# Quick Exercise

$$Y = \bar{A} \cdot \bar{B} \cdot C \cdot \bar{D} + \bar{A} \cdot B \cdot \bar{C} \cdot \bar{D} + \bar{A} \cdot B \cdot \bar{C} \cdot D + A \cdot B \cdot \bar{C} \cdot \bar{D} + A \cdot B \cdot \bar{C} \cdot D + A \cdot \bar{B} \cdot C \cdot \bar{D}$$

	$\bar{C} \cdot \bar{D}$	$\bar{C} \cdot D$	$C \cdot D$	$C \cdot \bar{D}$
$\bar{A} \cdot \bar{B}$	0	0	0	1
$\bar{A} \cdot B$	1	1	0	0
$A \cdot B$	1	1	0	0
$A \cdot \bar{B}$	0	0	0	1

- $B\bar{C} + \bar{B}C\bar{D}$

# Circuit Creation Algorithm

- Understand desired behaviour
- Write truth table
- Write SOM (or POM) for truth table
- Simplify SOM using K-Map
- Translate simplified SOM into Circuits
- Celebrate!