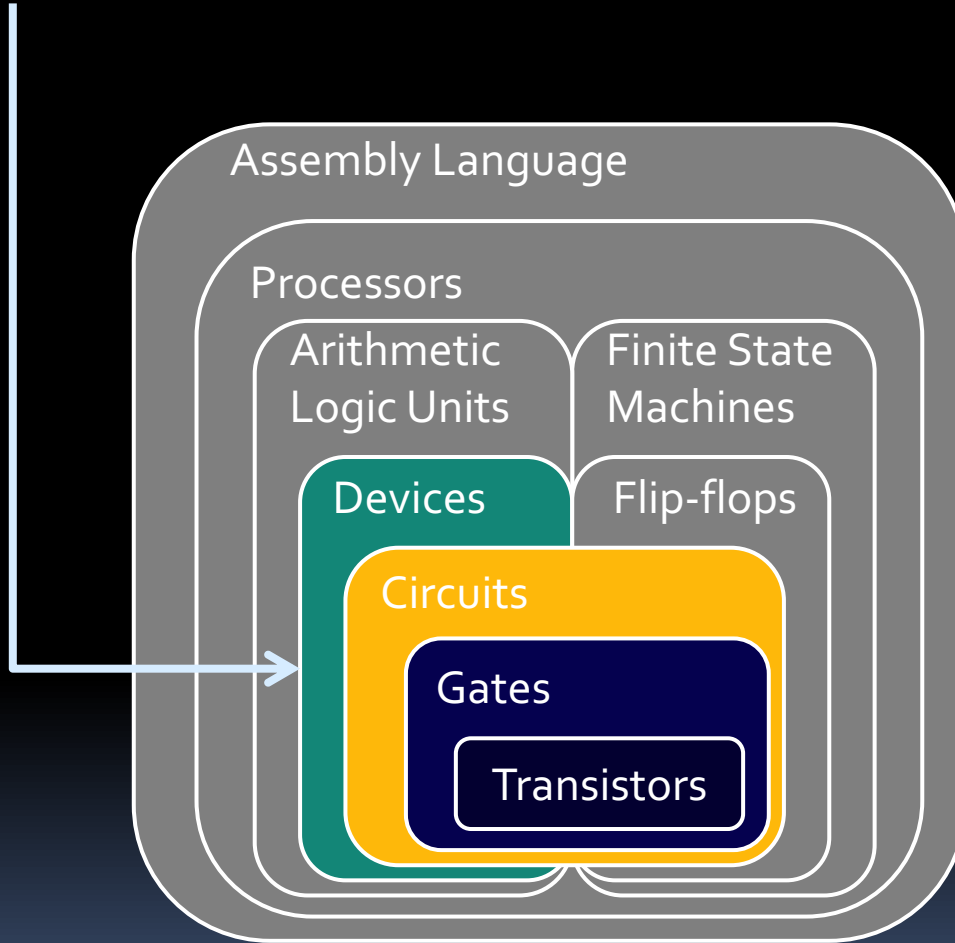



Week 3: Logical Devices

We are here



Building up from gates...

- Some common and more complex structures:
 - Multiplexers (MUX)
 - Adders (half and full)
 - Subtractors
 - Comparators
 - Decoders
 - Seven-segment decoders



These are all
**combinational
circuits**

Combinational Circuits

- *Combinational Circuits* are any circuits where the outputs rely strictly on the inputs.
 - Everything we've done so far and what we'll do today is all combinational logic.
- Another category is *sequential circuits* that we will learn in the next few weeks.

Karnaugh map review

	$\bar{B} \cdot \bar{C}$	$\bar{B} \cdot C$	$B \cdot C$	$B \cdot \bar{C}$
\bar{A}	0	0	1	0
A	1	0	1	1

- K-maps provide an illustration of a circuit's minterms (or maxterms), and a guide to how neighbouring terms may be combined.

$$\begin{aligned} Y &= \bar{A} \cdot B \cdot C + A \cdot \bar{B} \cdot \bar{C} + A \cdot B \cdot \bar{C} + A \cdot B \cdot C \\ &= B \cdot C + A \cdot \bar{C} \end{aligned}$$

Karnaugh map example

- Create a circuit with four inputs (A, B, C, D), and two outputs (X, Y):
 - The output X is high whenever two or more of the inputs are high.
 - The output Y is high when three or more of the inputs are high.

A	B	C	D	X	Y
0	0	0	0		
0	0	0	1		
0	0	1	0		
0	0	1	1		
0	1	0	0		
0	1	0	1		
0	1	1	0		
0	1	1	1		
1	0	0	0		
1	0	0	1		
1	0	1	0		
1	0	1	1		
1	1	0	0		
1	1	0	1		
1	1	1	0		
1	1	1	1		

Karnaugh map example

X:

	$\bar{C} \cdot \bar{D}$	$\bar{C} \cdot D$	$C \cdot D$	$C \cdot \bar{D}$
$\bar{A} \cdot \bar{B}$	0	0	1	0
$\bar{A} \cdot B$	0	1	1	1
$A \cdot B$	1	1	1	1
$A \cdot \bar{B}$	0	1	1	1

$$X = A \cdot B + C \cdot D + B \cdot D + B \cdot C + A \cdot D + A \cdot C$$

Alternative for X: Maxterms

X:

	$\bar{C} \cdot \bar{D}$	$\bar{C} \cdot D$	$C \cdot D$	$C \cdot \bar{D}$
$\bar{A} \cdot \bar{B}$	0	0	1	0
$\bar{A} \cdot B$	0	1	1	1
$A \cdot B$	1	1	1	1
$A \cdot \bar{B}$	0	1	1	1

Alternative for X: Maxterms

X:

	C+D	C+ \bar{D}	\bar{C} + \bar{D}	\bar{C} +D
A+B	0	0	1	0
A+ \bar{B}	0	1	1	1
\bar{A} + \bar{B}	1	1	1	1
\bar{A} +B	0	1	1	1

$$X = (A+C+D) \cdot (B+C+D) \cdot (A+B+C) \cdot (A+B+D)$$

Karnaugh map example


Y :

	$\bar{C} \cdot \bar{D}$	$\bar{C} \cdot D$	$C \cdot D$	$C \cdot \bar{D}$
$\bar{A} \cdot \bar{B}$	0	0	0	0
$\bar{A} \cdot B$	0	0	1	0
$A \cdot B$	0	1	1	1
$A \cdot \bar{B}$	0	0	1	0

$$Y = A \cdot B \cdot D + B \cdot C \cdot D + A \cdot B \cdot C + A \cdot C \cdot D$$

Karnaugh map review

 
- Note: There are cases where no combinations are possible. K-maps cannot help these cases.
- Example: Multi-input XOR gates.



	$\bar{B} \cdot \bar{C}$	$\bar{B} \cdot C$	$B \cdot C$	$B \cdot \bar{C}$
\bar{A}	0	1	0	1
A	1	0	1	0

$$Y = \bar{A} \cdot \bar{B} \cdot C + A \cdot \bar{B} \cdot \bar{C} + \bar{A} \cdot B \cdot \bar{C} + A \cdot B \cdot C$$


Multiplexers

 


Logic devices

- Certain structures are common to many circuits, and have block elements of their own.
 - e.g., Multiplexers (short form: **mux**)
 - Behaviour: Output is X if S is 0, and Y if S is 1:
 - S is the select input; X and Y are the data inputs.

n specifies the number of bits.

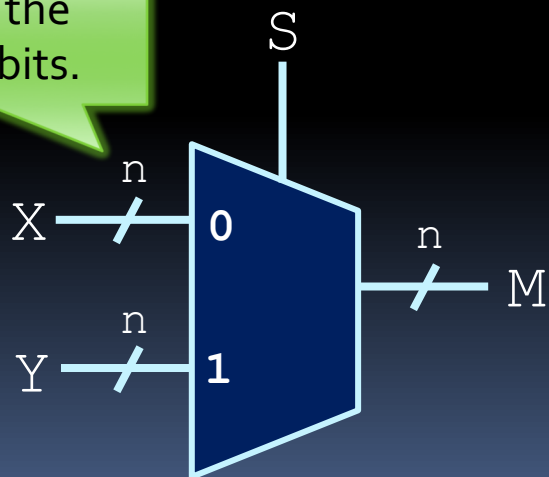

2-to-1 mux

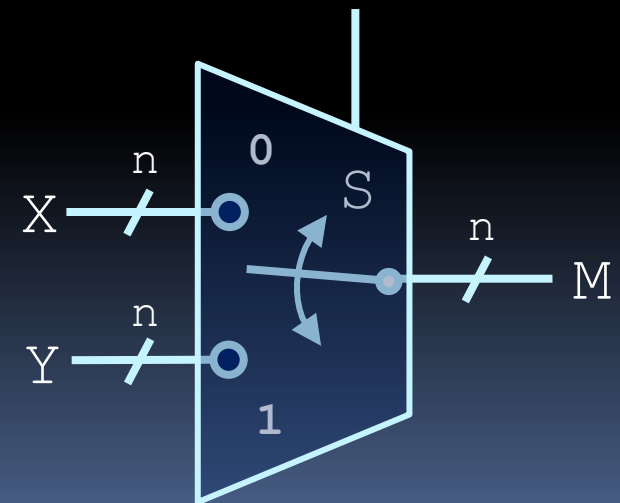

Multiplexer uses

- Muxes are very useful whenever you need to select from multiple input values.
- Your TV has at least one!
You can select different input sources.
- More examples:
 - surveillance video monitors
 - digital cable boxes
 - routers.



MPV-116A

Multiplexer design



X	Y	S	M
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Multiplexer design

X	Y	S	M
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

	$\bar{Y} \cdot \bar{S}$	$\bar{Y} \cdot S$	$Y \cdot S$	$Y \cdot \bar{S}$
\bar{X}	0	0	1	0
X	1	0	1	1

$$M = Y \cdot S + X \cdot \bar{S}$$

  


Decoders





Decoders

 - Decoders are essentially translators.
 - Translate from the output of one circuit to the input of another.
 - Think of them as **providing a mapping between two different encodings!**
- Example: Binary signal splitter
 - Activates one of four output lines, based on a two-digit binary number. (binary \rightarrow "one-hot")



Demultiplexers

 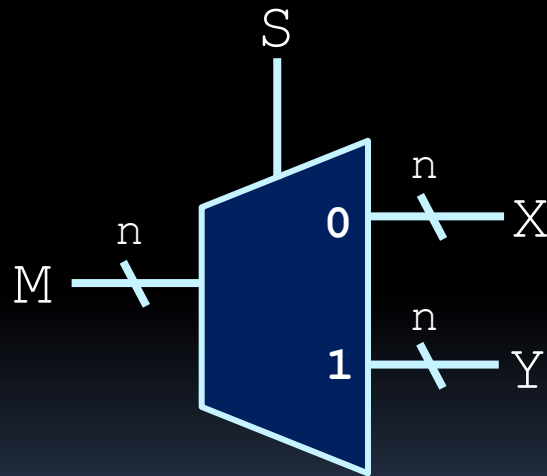- Related to decoders: demultiplexers.
 - Does multiplexer operation, in reverse.



7-segment decoder



- Common and useful decoder application.

- Translate from a 4-digit binary number to the seven segments of a digital display.


- Each output segment has a particular logic that defines it.

- Example: Segment 0


- Activate for values: 0, 2, 3, 5, 6, 7, 8, 9.

- In binary: 0000, 0010, 0011, 0101, 0110, 0111, 1000, 1001.

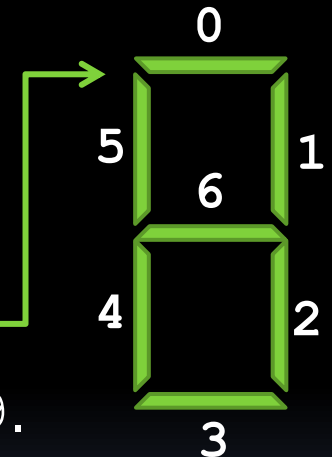- First step: Build the truth table and K-map.



7-segment decoder

 


- These segments are “**active-low**”, meaning that setting it low turns it on.
- Example: Displaying digits 0-9
 - Assume input is a 4-digit binary number
 - Segment 0 (top segment) is low whenever the input values are 0000, 0010, 0011, 0101, 0110, 0111, 1000 or 1001, and high whenever input number is 0001 or 0100 .
 - This create a truth table and map like the following....

7-segment decoder

x_3	x_2	x_1	x_0	HEX ₀
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0

	$\bar{x}_1 \cdot \bar{x}_0$	$\bar{x}_1 \cdot x_0$	$x_1 \cdot x_0$	$x_1 \cdot \bar{x}_0$
$\bar{x}_3 \cdot \bar{x}_2$	0	1	0	0
$\bar{x}_3 \cdot x_2$	1	0	0	0
$x_3 \cdot x_2$?	?	?	?
$x_3 \cdot \bar{x}_2$	0	0	?	?

 - $HEX_0 = \bar{x}_3 \cdot \bar{x}_2 \cdot \bar{x}_1 \cdot x_0 + \bar{x}_3 \cdot x_2 \cdot \bar{x}_1 \cdot \bar{x}_0$
- But what about input values from 1010 to 1111?



“Don’t care” values

- Input values that will never happen or are not meaningful in a given design, and so their output values do not have to be defined.
 - Recorded as 'X' in truth-tables and K-Maps.
- In the K-maps we can think of these “don’t care” values as either 0 or 1 depending on what helps us simplify our circuit.
 - Note you do **NOT** change the X with a 0 or 1, you just include it in a grouping as needed.


“Don’t care” values

- New equation for HEX0:

	$\bar{x}_1 \cdot \bar{x}_0$	$\bar{x}_1 \cdot x_0$	$x_1 \cdot x_0$	$x_1 \cdot \bar{x}_0$
$\bar{x}_3 \cdot \bar{x}_2$	0	1	0	0
$\bar{x}_3 \cdot x_2$	1	0	0	0
$x_3 \cdot x_2$	x	x	x	x
$x_3 \cdot \bar{x}_2$	0	0	x	x

$$\text{HEX0} = \bar{x}_3 \cdot \bar{x}_2 \cdot \bar{x}_1 \cdot x_0 \\ + x_2 \cdot \bar{x}_1 \cdot \bar{x}_0$$

Again for segment 1

 


x_3	x_2	x_1	x_0	HEX ₁
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0

	$\bar{x}_1 \cdot \bar{x}_0$	$\bar{x}_1 \cdot x_0$	$x_1 \cdot x_0$	$x_1 \cdot \bar{x}_0$
$\bar{x}_3 \cdot \bar{x}_2$	0	0	0	0
$\bar{x}_3 \cdot x_2$	0	1	0	1
$x_3 \cdot x_2$	x	x	x	x
$x_3 \cdot \bar{x}_2$	0	0	x	x

$$\text{HEX1} = x_2 \cdot \bar{x}_1 \cdot x_0 + x_2 \cdot x_1 \cdot \bar{x}_0$$

Again for segment 2

 


x_3	x_2	x_1	x_0	HEX ₂
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0

	$\bar{x}_1 \cdot \bar{x}_0$	$\bar{x}_1 \cdot x_0$	$x_1 \cdot x_0$	$x_1 \cdot \bar{x}_0$
$\bar{x}_3 \cdot \bar{x}_2$	0	0	0	1
$\bar{x}_3 \cdot x_2$	0	0	0	0
$x_3 \cdot x_2$	x	x	x	x
$x_3 \cdot \bar{x}_2$	0	0	x	x

HEX2 = $\bar{x}_2 \cdot x_1 \cdot \bar{x}_0$

The final 7-seg decoder

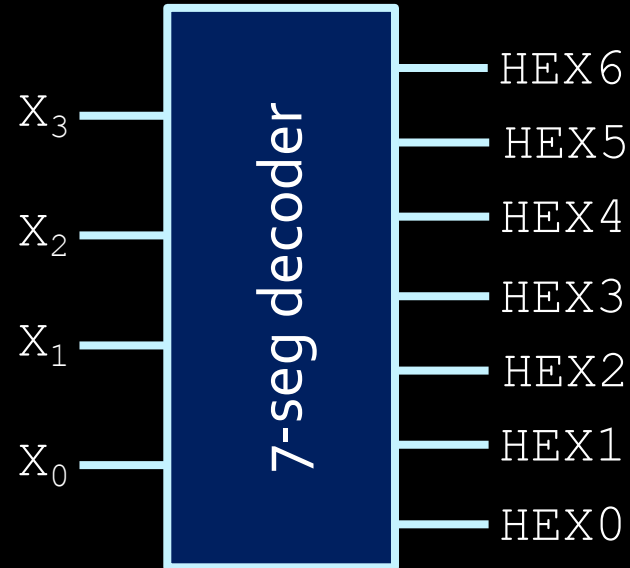- There are many kinds of decoders.
- They all look the same, except for the inputs and outputs.
- Of course, unlike other devices, the internals differs from decoder to decoder.



Another “don’t care” example


- Climate control fan:
 - The fan should turn on (F) if the temperature is hot (H) or if the temperature is cold (C), depending on whether the unit is set to A/C or heating (A).

H	C	A	F
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

	$\bar{H} \cdot \bar{C}$	$\bar{H} \cdot C$	$H \cdot C$	$H \cdot \bar{C}$
\bar{A}	0	1	X	0
A	0	0	X	1

$$F = A \cdot H + \bar{A} \cdot C$$

Adder circuits

 

Adders

- Also known as binary adders.
 - Small circuit devices that add two digits together.
 - Combined together to create **iterative combinational circuits**.
- Types of adders:
 - Half adders (HA)
 - Full adders (FA)
 - Ripple Carry Adder
 - Carry-Look-Ahead Adder (CLA)



Review of Binary Math

- Each digit of a decimal number represents a power of 10:

$$258 = 2 \times 10^2 + 5 \times 10^1 + 8 \times 10^0$$

- Each digit of a binary number represents a power of 2:

$$\begin{aligned} 01101_2 &= 0 \times 2^4 + 1 \times 2^3 + 1 \times 2^2 + 0 \times 2^1 + 1 \times 2^0 \\ &= 13_{10} \end{aligned}$$

Unsigned binary addition

- $27 + 53$

$$27 = 00011011$$

$$53 = 00110101$$



1 1 1 1 1 1

00011011

+00110101



01010000



80₁₀

01010000

Unsigned binary addition

▪ $27 + 53$

$27 = 00011011$

$53 = 00110101$



1 1 1 1 1 1

00011011

+00110101

01010000



80_{10}

01010000

▪ $95 + 181$

01011111

+10110101



1 1 1 1 1 1 1 1

01011111

+10110101

100010100

carry bit



$20_{10} ??$



00010100

With 8 bits we can only represent unsigned numbers 0 to 255 !


Half Adders

- A 2-input, 1-bit width binary adder that performs the following computations:

X	0	0	1	1
+Y	+0	+1	+0	+1
<hr/>	<hr/>	<hr/>	<hr/>	<hr/>
CS	00	01	01	10

This is a truth table!

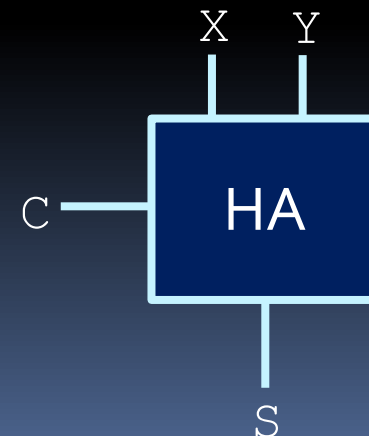
- A half adder adds two bits to produce a two-bit sum.
- The sum is expressed as a sum bit S and a carry bit C.




Half Adder Implementation

- Equations and circuits for half adder units are easy to define (even without Karnaugh maps)
 
$$C = X \cdot Y \quad S = X \cdot \bar{Y} + \bar{X} \cdot Y \\ = X \oplus Y$$



Full Adders

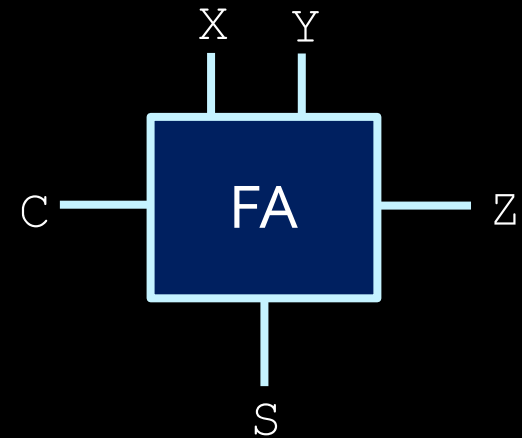

- Similar to half-adders, but with another input Z , which represents a carry-in bit.
 - C and Z are sometimes labeled as C_{out} and C_{in} .
- When Z is 0, the unit behaves exactly like a half adder.
- When Z is 1:

X	0	0	1	1
+Y	+0	+1	+0	+1
+Z	+1	+1	+1	+1
<hr/>	<hr/>	<hr/>	<hr/>	<hr/>
CS	01	10	10	11

Full Adder Design

X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

C	$\bar{Y} \cdot \bar{Z}$	$\bar{Y} \cdot Z$	$Y \cdot Z$	$Y \cdot \bar{Z}$
\bar{X}	0	0	1	0
X	0	1	1	1

S	$\bar{Y} \cdot \bar{Z}$	$\bar{Y} \cdot Z$	$Y \cdot Z$	$Y \cdot \bar{Z}$
\bar{X}	0	1	0	1
X	1	0	1	0

$$C = X \cdot Y + X \cdot Z + Y \cdot Z$$


$$S = X \oplus Y \oplus Z$$

Full Adder Design

- The C term can also be rewritten as:


$$C = X \cdot Y + (X \oplus Y) \cdot Z$$

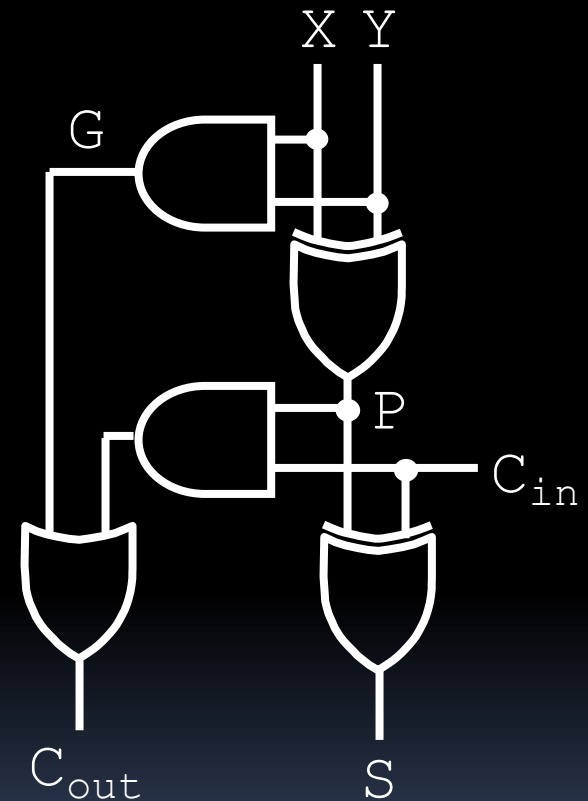- Two terms come from this:
 - $X \cdot Y =$ carry generate (G).
 - $X \oplus Y =$ carry propagate (P).
- Results in this circuit →



Ripple-Carry Binary Adder

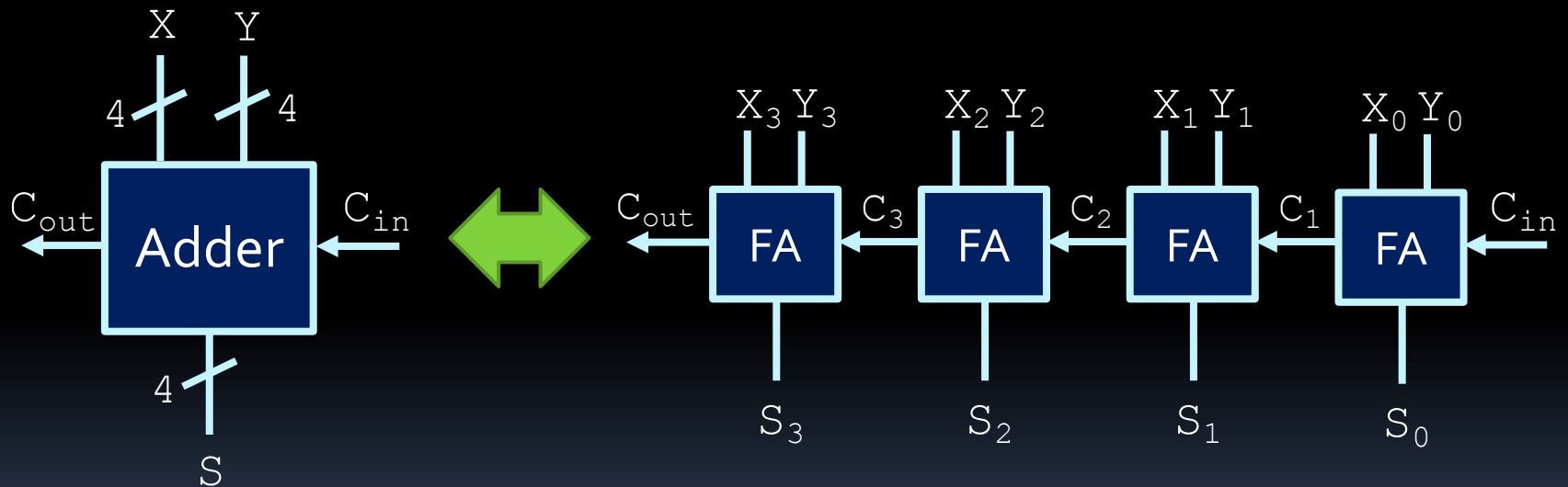- Full adder units are chained together in order to perform operations on signal **vectors**.




Break



The role of C_{in}

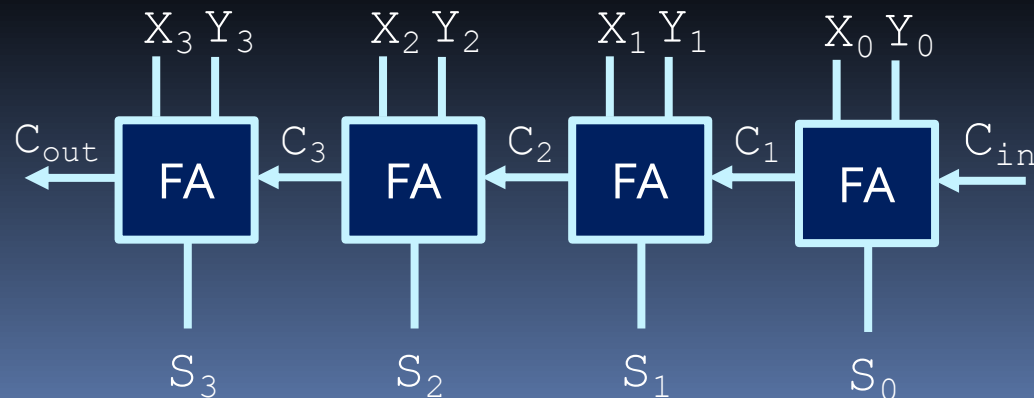- Why can't we just have a half-adder for the smallest (right-most) bit?
- We could, if we were only interested in addition. But the last bit allows us to do subtraction as well!
 - Time for a little fun with subtraction!



Lets Have Fun

1. Find a partner.
2. Have each person choose a **five-digit binary number**.
3. Take the **smaller number**, and invert all the digits.
4. Add this inverted number to the larger one.
5. **Add one to the result**.
6. Check what the result is...



Subtractors

- Subtractors are an extension of adders.
 - Basically, perform addition on a negative number.
- To do subtraction, we need to understand representation of negative binary numbers.
- **Unsigned numbers**
 - Data bits store the positive version of the number.
- **Sign-and-magnitude**
 - Another, separate bit exists for the sign (the sign bit).
- **Signed:**
 - Store a **2's complement** negative number using all bits.
 - More common, and **what we use for this course**.

Two's complement

- Need to know how to get **1's complement**:
 - Given number X with n bits, take $(2^n - 1) - X$
 - Invert individual bits (bitwise NOT).

01001101	→	10110010
11111111	→	00000000

- **2's complement = (1's complement + 1)**

01001101	→	10110011
11111111	→	00000001

Know
this!

- Note: Adding a 2's complement number to the original number produces a result of **zero**.

Signed representations

Decimal	Unsigned	Signed 2's
7	111	---
6	110	---
5	101	---
4	100	---
3	011	011
2	010	010
1	001	001
0	000	000
-1	---	111
-2	---	110
-3	---	101
-4	---	100

Practice 2's complement!

- Assume 4-bits signed representation, write the following decimal numbers in binary:

□ 2 => 0010

□ -1 => 1111

□ 0 => 0000

□ 8 => Not possible to represent in 4 digits!

□ -8 => 1000

- What is max positive number?

=> 7 (or $2^{4-1} - 1$)

- What is min negative number?

=> -8 (or -2^{4-1})

Rules about signed numbers

- When thinking of signed binary numbers, there are a few useful rules to remember:
 - The largest positive binary number is a zero followed by all ones.
 - The binary value for -1 has ones in all the digits.
 - The most negative binary number is a one followed by all zeroes.
- There are 2^n possible values that can be stored in an n -digit binary number.
 - 2^{n-1} are negative, $2^{n-1}-1$ are positive, and one is zero.
 - For example, given an 8-bit binary number:
 - There are 256 possible values
 - One of those values is zero
 - 128 are negative values (11111111 to 10000000)
 - 127 are positive values (00000001 to 01111111)

-1 to -128

1 to 127



Signed subtraction

- Negative numbers are generally stored in 2's complement notation.
 - Reminder: 1's complement \rightarrow bits are the bitwise NOT of the equivalent positive value.
 - 2's complement \rightarrow 1's complement value plus one; results in zero when added to equivalent positive value.
- Subtraction can then be performed by **using the binary adder circuit with negative numbers.**

At the core of subtraction

- Subtraction of a number is simply the addition of its negative value.
- This the negative value is found using the 2's complement process.
 - $7 - 3 = 7 + (-3)$
 - $-3 - 2 = -3 + (-2)$

Signed Subtraction example

▪ $7 - 3$

$$\begin{array}{r} 0111 \\ -0011 \\ \hline \end{array}$$



$$0111$$

discarded $+1101$

$$\begin{array}{r} 10100 \\ \hline \end{array}$$



$$0100 = 4_{10}$$

▪ $-3 - 2$

$$\begin{array}{r} 1101 \\ -0010 \\ \hline \end{array}$$



$$1101$$

discarded $+1110$

$$\begin{array}{r} 11011 \\ \hline \end{array}$$



$$1011 = -5_{10}$$

What about bigger numbers

▪ $53 - 27$

$$\begin{array}{r} 00110101 \\ -00011011 \\ \hline \end{array}$$



$$00110101$$

discarded

$$\begin{array}{r} +11100101 \\ \hline 100011010 \end{array}$$



$$00011010 = 26_{10}$$

▪ $27 - 53$

$$\begin{array}{r} 00011011 \\ -00110101 \\ \hline \end{array}$$



$$00011011$$

discarded

$$\begin{array}{r} +11001011 \\ \hline 011100110 \end{array}$$




$$11100110 = -26_{10}$$

Subtraction circuit


- 4-bit subtractor: $X - Y$
 - X plus 2's complement of Y
 - X plus 1's complement of Y plus 1

Feed 1 as Carry-In in the least significant FA.

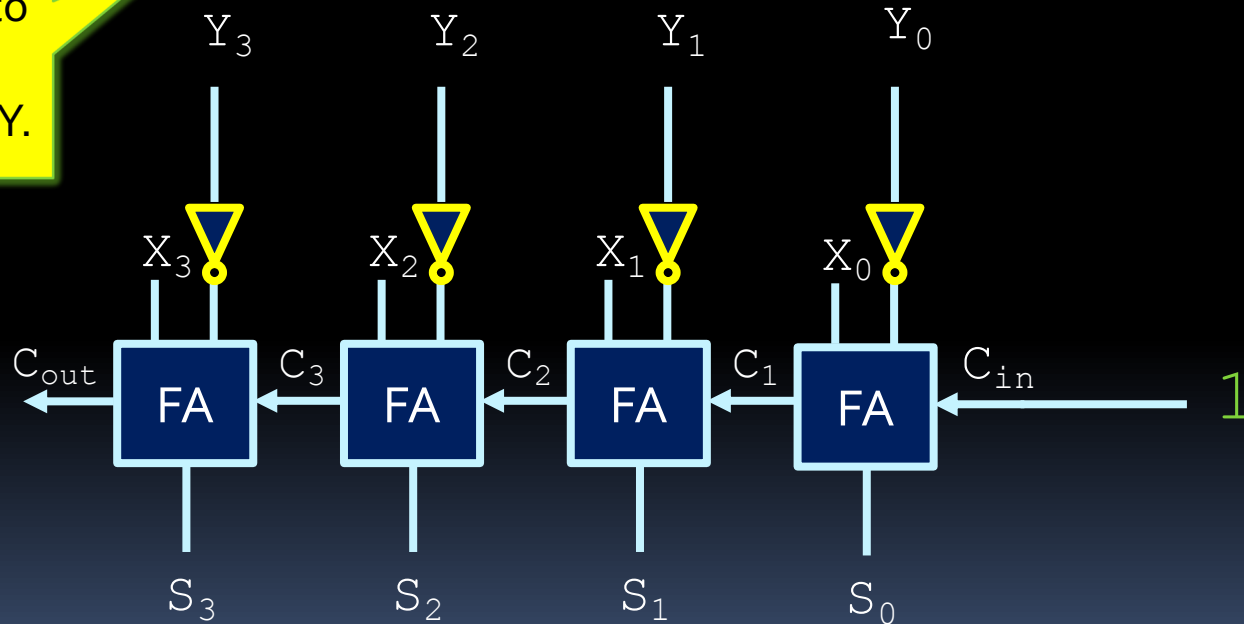Use NOT gates to get the 1's complement of Y .



Addition/Subtraction circuit

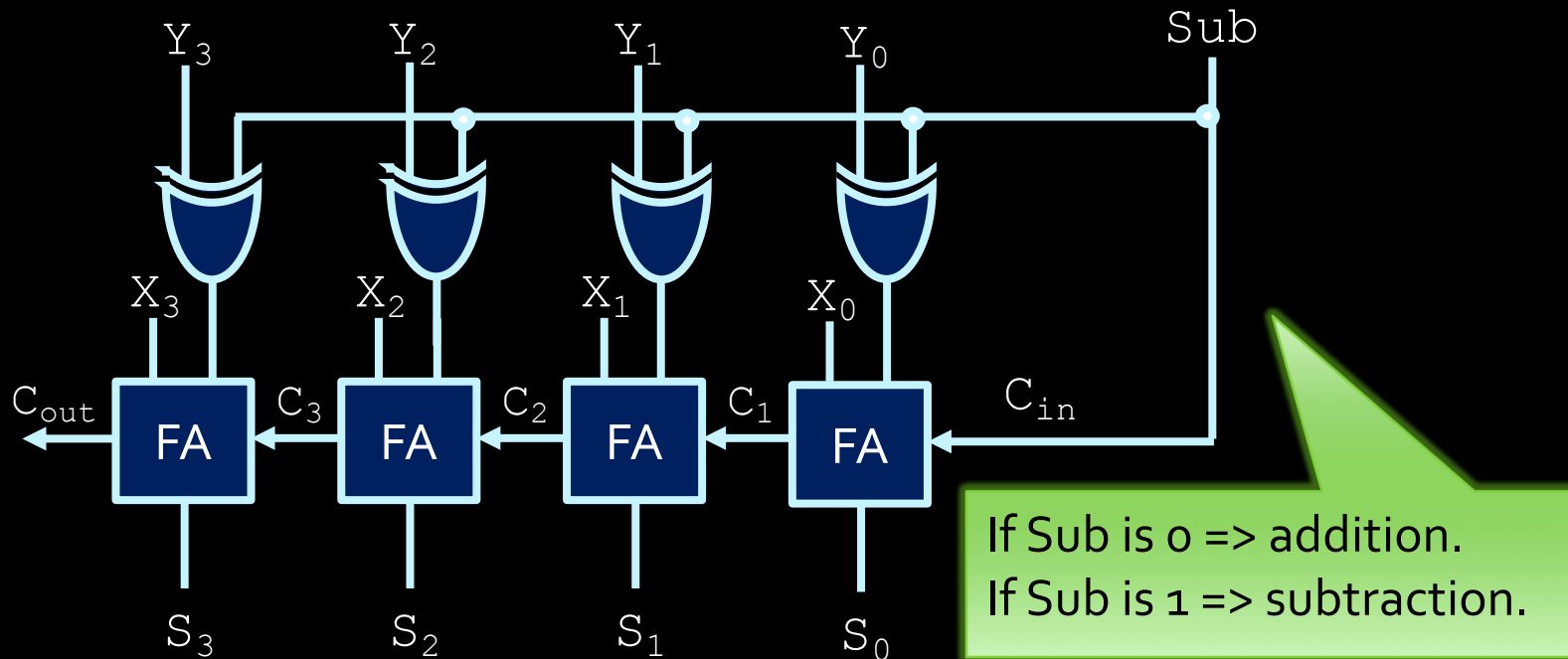

- The full adder circuit can be expanded to incorporate the subtraction operation
 - Remember: 2's complement = 1's complement + 1
 - We connect Sub to C_{in}

Food for Thought

- What happens if we add these two positive signed binary numbers $0110 + 0011$ (i.e., $6 + 3$)?
 - The result is 1001 .
 - But that is a negative number (-7)! ☹️
- What happens if we add the two negative numbers $1000 + 1111$ (i.e., $-8 + (-1)$)?
 - The result is 0111 with a carry-out. ☹️
- We need to know when the result might be wrong.
 - This is usually indicated in hardware by the **Overflow** flag!
 - More about this when we'll talk about processors.

Subtracting unsigned numbers

- General algorithm for $X - Y$:
 1. Get the 2's complement of the subtrahend Y (the term being subtracted).
 2. Add that value to the minuend X (the term being subtracted from).
 3. If there is an end carry (C_{out} is high), the final result is positive and does not change.
 4. If there is no end carry (C_{out} is low), get the 2's complement of the result and add a negative sign to it (or set the sign bit high).

Unsigned subtraction example

▪ $53 - 27$

$$\begin{array}{r} 00110101 \\ -00011011 \\ \hline \end{array}$$



▪ $27 - 53$

$$\begin{array}{r} 00011011 \\ -00110101 \\ \hline \end{array}$$



Unsigned subtraction example

▪ $53 - 27$

$$\begin{array}{r} 00110101 \\ -00011011 \\ \hline \end{array}$$



$$00110101$$

carry bit

$$+11100101$$

$$\begin{array}{r} \boxed{1}00011010 \\ \hline \end{array}$$



$$00011010$$

sign bit
is low

▪ $27 - 53$

$$\begin{array}{r} 00011011 \\ -00110101 \\ \hline \end{array}$$



$$00011011$$

no carry bit

$$+11001011$$

$$\begin{array}{r} \boxed{0}11100110 \\ \hline \end{array}$$



$$-00011010$$

sign bit
is high

Comparators




Comparators

- A circuit that takes in two input vectors, and determines if the first is greater than, less than or equal to the second.
- How does one make that in a circuit?



Basic Comparators

 

- Consider two binary numbers A and B, where A and B are one bit long.
- The circuits for this would be:

□ A==B:

$$A \cdot B + \bar{A} \cdot \bar{B}$$

□ A>B:

$$A \cdot \bar{B}$$


□ A<B:

$$\bar{A} \cdot B$$

A	B
0	0
0	1
1	0
1	1

Basic Comparators

 - What if A and B are two bits long?
- The terms for this circuit for have to expand to reflect the second signal.
- For example:




□ $A==B$:

$$(A_1 \cdot B_1 + \bar{A}_1 \cdot \bar{B}_1) \cdot (A_0 \cdot B_0 + \bar{A}_0 \cdot \bar{B}_0)$$

Make sure that the values
of bit 1 are the same

Make sure that the values
of bit 0 are the same

Basic Comparators

 

- What about checking if A is greater or less than B?

□ $A>B$:

$$A_1 \cdot \bar{B}_1 + (A_1 \cdot B_1 + \bar{A}_1 \cdot \bar{B}_1) \cdot (A_0 \cdot \bar{B}_0)$$

Check if first bit satisfies condition


If not, check that the first bits are equal...

...and then do the 1-bit comparison

□ $A<B$:

$$\bar{A}_1 \cdot B_1 + (A_1 \cdot B_1 + \bar{A}_1 \cdot \bar{B}_1) \cdot (\bar{A}_0 \cdot B_0)$$

Basic Comparators

 

- The final circuit equations for two-input comparators are shown below.
 - Note the sections they have in common!

□ $A==B:$

$$(A_1 \cdot B_1 + \bar{A}_1 \cdot \bar{B}_1) \cdot (A_0 \cdot B_0 + \bar{A}_0 \cdot \bar{B}_0)$$

□ $A>B:$

$$A_1 \cdot \bar{B}_1 + (A_1 \cdot B_1 + \bar{A}_1 \cdot \bar{B}_1) \cdot (A_0 \cdot \bar{B}_0)$$

□ $A<B:$

$$\bar{A}_1 \cdot B_1 + (A_1 \cdot B_1 + \bar{A}_1 \cdot \bar{B}_1) \cdot (\bar{A}_0 \cdot B_0)$$

General Comparators

- The general circuit for comparators requires you to define equations for each case.
- Case #1: Equality
 - If inputs A and B are equal, then all bits must be the same.
 - Define X_i for any digit i :
 - (equality for digit i)
 - Equality between A and B is defined as:

$$X_i = A_i \cdot B_i + \bar{A}_i \cdot \bar{B}_i$$

$$A==B : X_0 \cdot X_1 \cdot \dots \cdot X_n$$

Comparators

- Case #2: $A > B$

- The first non-matching bits occur at bit i , where $A_i=1$ and $B_i=0$. All higher bits match.
- Using the definition for X_i from before:

$$A > B = A_n \cdot \bar{B}_n + X_n \cdot A_{n-1} \cdot \bar{B}_{n-1} + \dots + A_0 \cdot \bar{B}_0 \cdot \prod_{k=1}^n X_k$$

- Case #3: $A < B$

- The first non-matching bits occur at bit i , where $A_i=0$ and $B_i=1$. Again, all higher bits match.

$$A < B = \bar{A}_n \cdot B_n + X_n \cdot \bar{A}_{n-1} \cdot B_{n-1} + \dots + \bar{A}_0 \cdot B_0 \cdot \prod_{k=1}^n X_k$$

Example for 4 bits

A=B

$$A=B = X_3 \cdot X_2 \cdot X_1 \cdot X_0$$

A > B

$$A_3 \cdot \bar{B}_3 + X_3 \cdot A_2 \cdot \bar{B}_2 + X_3 \cdot X_2 \cdot A_1 \cdot \bar{B}_1 + X_3 \cdot X_2 \cdot X_1 \cdot A_0 \cdot \bar{B}_0$$

A < B

$$\bar{A}_3 \cdot B_3 + X_3 \cdot \bar{A}_2 \cdot B_2 + X_3 \cdot X_2 \cdot \bar{A}_1 \cdot B_1 + X_3 \cdot X_2 \cdot X_1 \cdot \bar{A}_0 \cdot B_0$$

Comparator truth table

- Given two input vectors of size $n=2$, output of circuit is shown at right.

Inputs				Outputs		
A_1	A_0	B_1	B_0	$A < B$	$A = B$	$A > B$
0	0	0	0	0	1	0
0	0	0	1	1	0	0
0	0	1	0	1	0	0
0	0	1	1	1	0	0
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	1	0	0
0	1	1	1	1	0	0
1	0	0	0	0	0	1
1	0	0	1	0	0	1
1	0	1	0	0	1	0
1	0	1	1	1	0	0
1	1	0	0	0	0	1
1	1	0	1	0	0	1
1	1	1	0	0	0	1
1	1	1	1	0	1	0

Comparator example (cont'd)

$A < B$:

	$\bar{B}_0 \cdot \bar{B}_1$	$B_0 \cdot \bar{B}_1$	$B_0 \cdot B_1$	$\bar{B}_0 \cdot B_1$
$\bar{A}_0 \cdot \bar{A}_1$	0	1	1	1
$A_0 \cdot \bar{A}_1$	0	0	1	1
$A_0 \cdot A_1$	0	0	0	0
$\bar{A}_0 \cdot A_1$	0	0	1	0

$$LT = B_1 \cdot \bar{A}_1 + B_0 \cdot B_1 \cdot \bar{A}_0 + B_0 \cdot \bar{A}_0 \cdot \bar{A}_1$$

Comparator example (cont'd)

$A=B$:

	$\bar{B}_0 \cdot \bar{B}_1$	$B_0 \cdot \bar{B}_1$	$B_0 \cdot B_1$	$\bar{B}_0 \cdot B_1$
$\bar{A}_0 \cdot \bar{A}_1$	1	0	0	0
$A_0 \cdot \bar{A}_1$	0	1	0	0
$A_0 \cdot A_1$	0	0	1	0
$\bar{A}_0 \cdot A_1$	0	0	0	1

$$EQ = \bar{B}_0 \cdot \bar{B}_1 \cdot \bar{A}_0 \cdot \bar{A}_1 + B_0 \cdot \bar{B}_1 \cdot A_0 \cdot \bar{A}_1 + B_0 \cdot B_1 \cdot A_0 \cdot A_1 + \bar{B}_0 \cdot B_1 \cdot \bar{A}_0 \cdot A_1$$

Comparator example (cont'd)

$A > B$:

	$\bar{B}_0 \cdot \bar{B}_1$	$B_0 \cdot \bar{B}_1$	$B_0 \cdot B_1$	$\bar{B}_0 \cdot B_1$
$\bar{A}_0 \cdot \bar{A}_1$	0	0	0	0
$A_0 \cdot \bar{A}_1$	1	0	0	0
$A_0 \cdot A_1$	1	1	0	1
$\bar{A}_0 \cdot A_1$	1	1	0	0

$$GT = \bar{B}_1 \cdot A_1 + \bar{B}_0 \cdot \bar{B}_1 \cdot A_1 + \bar{B}_0 \cdot A_0 \cdot A_1$$

Comparators in Verilog

- Implementing a comparator can be done by putting together the circuits as shown in the previous slide, or by using the comparison operators to make things a little easier:

```
module comparator_4_bit (a_gt_b, a_lt_b, a_eq_b, a, b);  
  
    input [3:0] a, b;  
    output a_gt_b, a_lt_b, a_eq_b;  
  
    assign a_gt_b = (a > b);  
    assign a_lt_b = (a < b);  
    assign a_eq_b = (a == b);  
  
endmodule
```

Comparing larger numbers

- As numbers get larger, the comparator circuit gets more complex.
- At a certain level, it can be easier sometimes to just process the result of a subtraction operation instead.
 - Easier, less circuitry, just not faster.

