
 


Lecture 4: Sequential Circuits Continued

Clock signals

 - “Clocks” are a regular pulse signal, where the high value indicates that the output of the latch may be sampled.
- Usually drawn as:




- But looks more like:




Signal restrictions

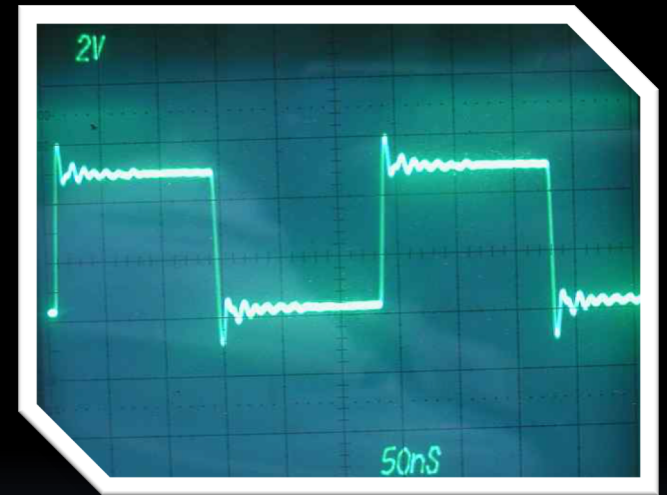- What's the limit to how fast the latch circuit can be sampled?
- Determined by:
 - latency time of transistors
 - Setup and hold time
 - setup time for clock signal
 - Jitter
 - Gibbs phenomenon
- **Frequency** = how many pulses occur per second, measured in Hertz (or Hz).




Clocked SR latch

 

- Adding another layer of NAND gates to the $\bar{S}\bar{R}$ latch gives us a **clocked SR latch** or gated SR latch)
 - Basically, a latch with a control input signal C.
- The input C is often connected to a pulse signal that alternates regularly between 0 and 1 (clock)


Clocked SR latch behaviour

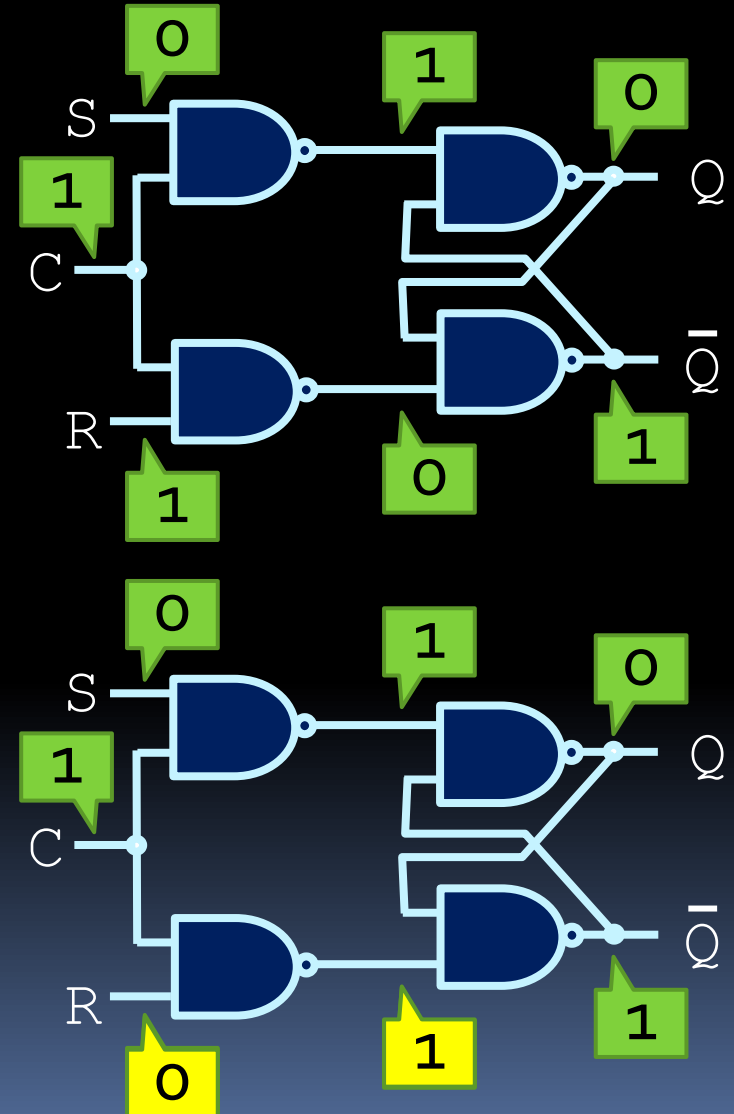- Same behaviour as SR latch, but with timing:
 - Start off with $S=0$ and $R=1$, like earlier example.
 - If clock is high, the first NAND gates invert those values, which get inverted again in the output.
 - Setting both inputs to 0 maintains the output values.




Clocked SR latch behaviour

 - Continued from previous:
 - Now set the clock low.
 - Even if the inputs change, the low clock input prevents the change from reaching the second stage of NAND gates.
 - Result: the clock needs to be high in order for the inputs to have any effect.




Clocked SR latch

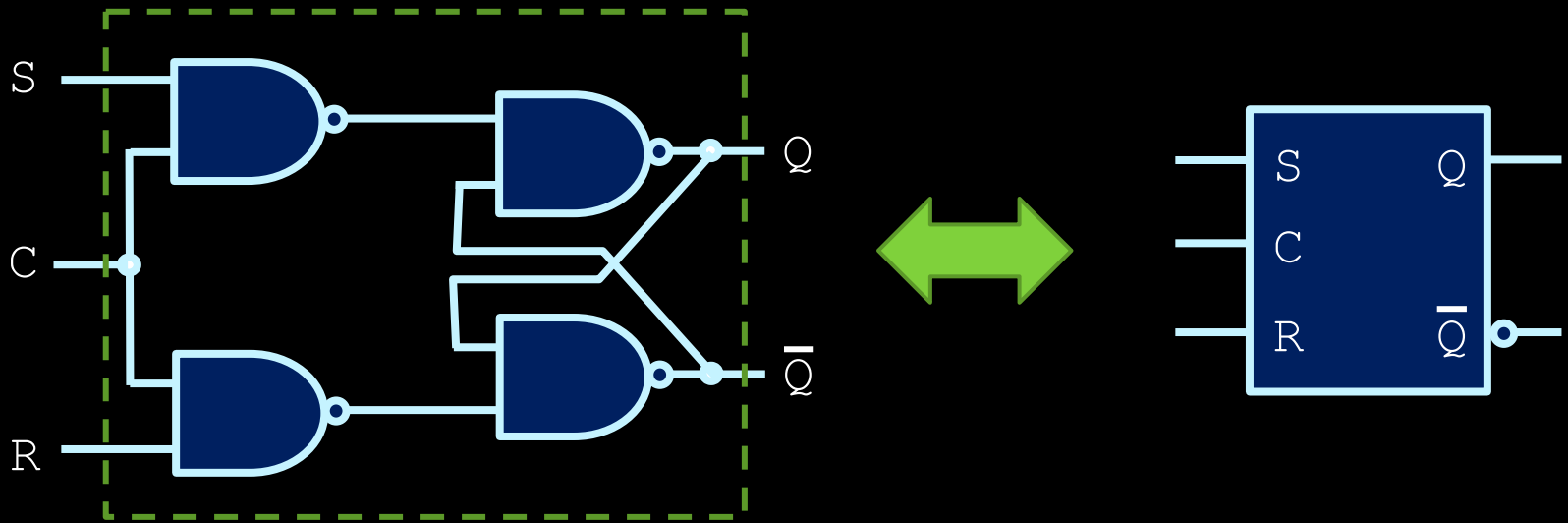

- This is the typical symbol for a clocked SR latch.
- **This only allows the S and R signals to affect the circuit when the clock input (C) is high.**
- Note: the small NOT circle after the \bar{Q} output is simply the notation to use to denote the inverted output value. It's not an extra NOT gate.


Clocked SR latch behaviour

 

Q_T	S	R	Q_{T+1}	Result
0	0	0	0	no change
0	0	1	0	reset
0	1	0	1	set
0	1	1	?	???
1	0	0	1	no change
1	0	1	0	reset
1	1	0	1	set
1	1	1	?	???

- Wait!
- Where's the clock?
- There's a better way to look at this....


Clocked SR latch behaviour

 

C	S	R	Q_{T+1}	Result
0	X	X	Q_T	no change
1	0	0	Q_T	no change
1	0	1	0	reset
1	1	0	1	set
1	1	1	?	Undefined

- Assuming the clock is 1, we still have a problem when S and R are both 1, since the state of Q is indeterminate.
 - Better design: prevent S and R from both going high.


D latch

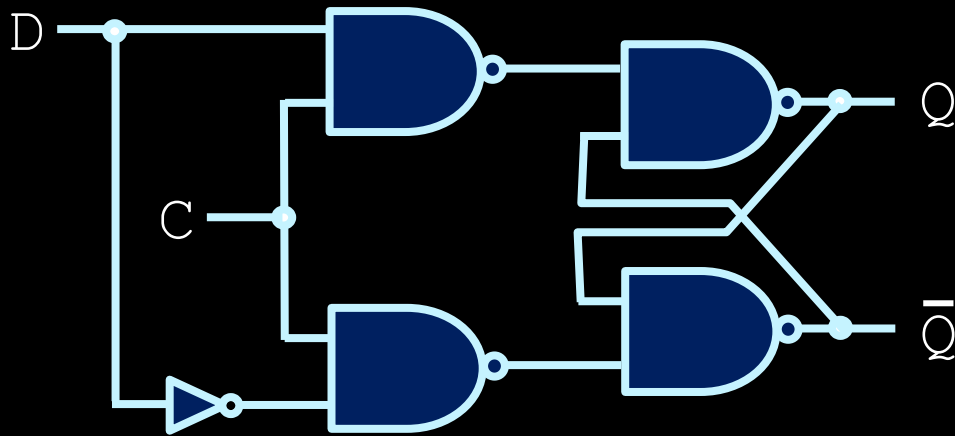

Q_T	D	Q_{T+1}
0	0	0
0	1	1
1	0	0
1	1	1

- By making the inputs to R and S dependent on a single signal D, you avoid the indeterminate state problem.
- The value of D now sets output Q low or high whenever C is high.


D latch

 


- This design is good, but still has problems.
 - i.e. **timing issues**.
 - How can we maintain state?

Latch timing issues

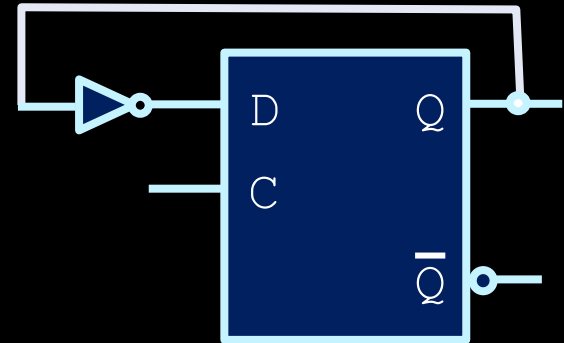- Consider the circuit on the right:
- When the clock signal is high, the output looks like the waveform below:




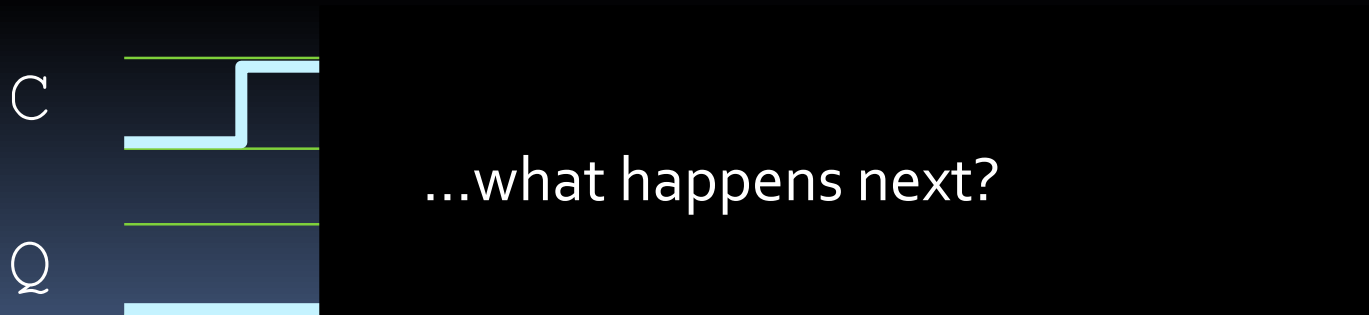- **Output keeps toggling back and forth.**




Latch timing issues

 - Consider the circuit on the right:
- When the clock signal is high, the output looks like the waveform below:



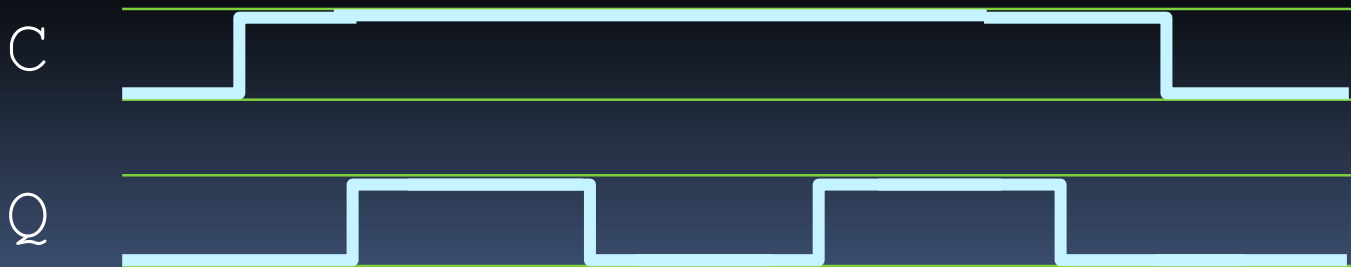- **Output keeps toggling back and forth.**




D-Latch is transparent!

- **Transparent** means that
 - Any changes to its inputs are visible to the output when control signal (Clock) is 1.
- **Key Take-away:** The “output of a latch **should not** be applied directly or through combinational logic to the input of the same or another latch when they all have the same control (clock) signal.”


Latch timing issues

 - Preferable behaviour:
 - Have output change only once when the clock pulse changes.
 - Solution: create **disconnect between circuit output and circuit input**, to prevent unwanted feedback and changes to output.





SR master-slave flip-flop

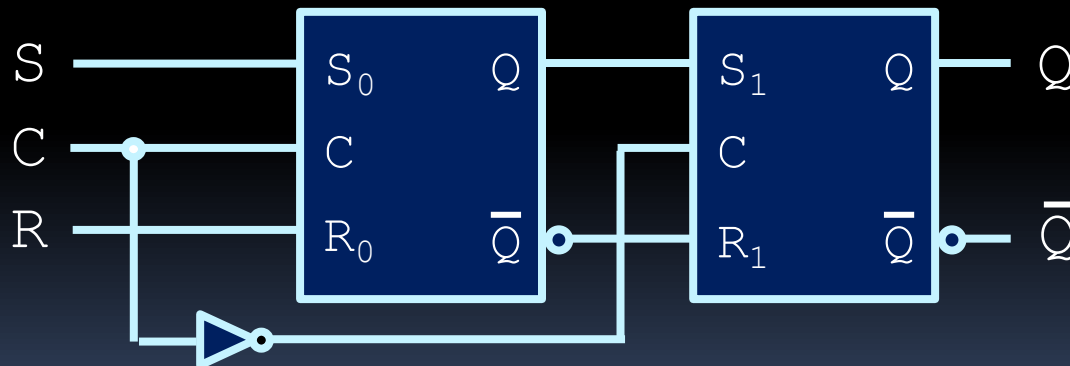- A **flip-flop** is a latched circuit whose output is triggered with the rising edge or falling edge of a clock pulse.
- Example: The SR master-slave flip-flop




SR master-slave flip-flop

  

propagation delay



Edge-triggered D flip-flop

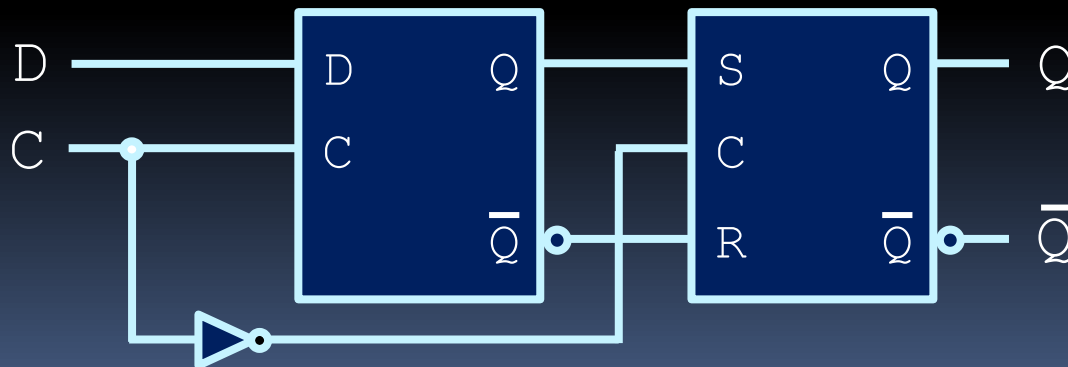- SR flip-flops still have issues of unstable behaviour.
- Solution: **D flip-flop**
 - Connect D latch to the input of a SR latch.
 - **Negative-edge triggered** flip-flop (like the SR)





Flip-flop behaviour

 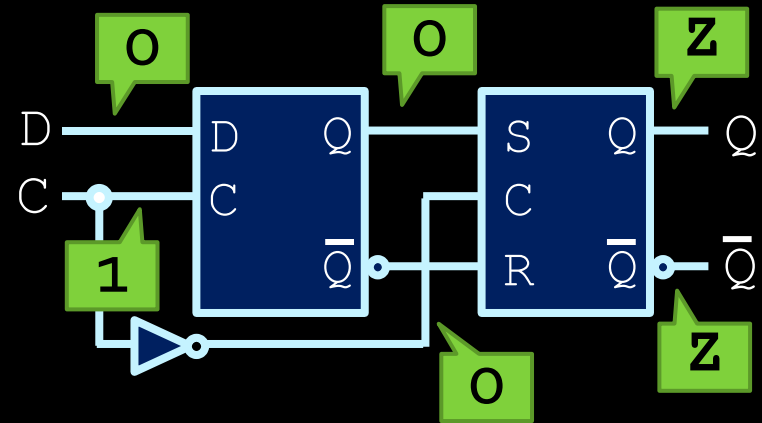- Observe the behaviour:
 - If the clock signal is high, the input to the first flip-flop is sent out to the second.
 - The second flip-flop doesn't do anything until the clock signal goes down again.
 - When it clock goes from high to low, the first flip-flop stops transmitting a signal, and the second one starts.




Flip-flop behaviour

  - Continued from previous:
 - If the input to D changes, the change isn't transmitted to the second flip-flop until the clock goes high again.
 - Once the clock goes high, the first flip-flop starts transmitting at the same time as the second flip-flop stops.




Confused yet?

- Maybe a demonstration will help

 

Edge-triggered flip-flop

 
- Alternative: **positive-edge triggered** flip-flops




- These are the most commonly-used flip-flop circuits (and our choice for the course).

Notation


- Latches

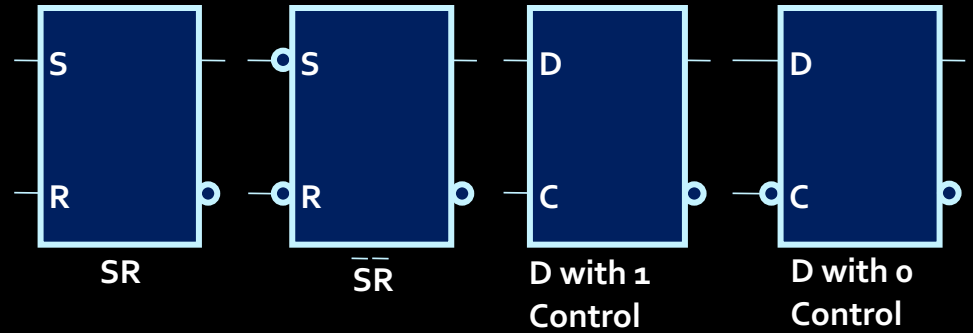

- Master-slave flip-flops

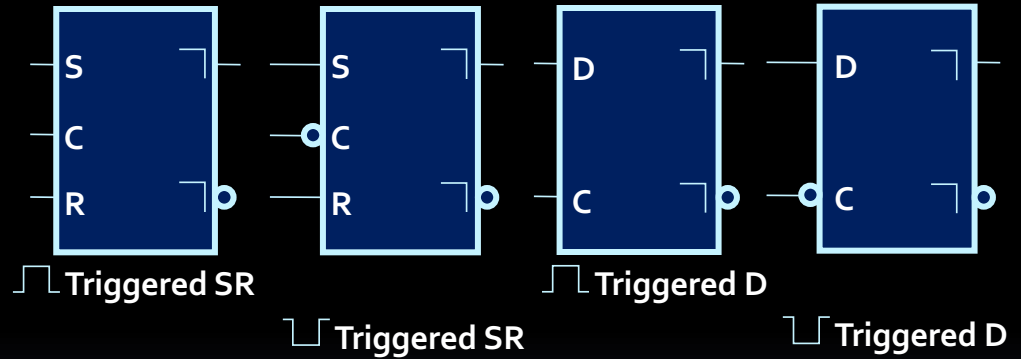


- Edge-triggered flip-flops

 

Note: While all these are possible, we mainly use edge-triggered D flip-flops in our designs.

Other Flip-Flops

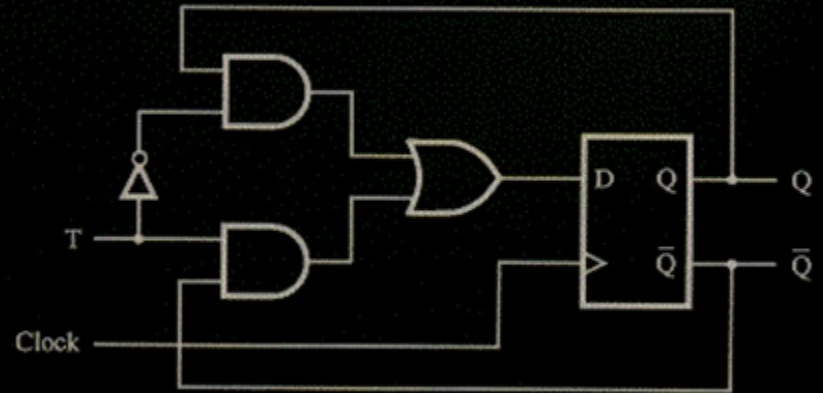- The **T flip-flop**:
 - Like the D flip-flop, except that it **toggles** its value whenever the input to T is high.




Other Flip-Flops

- The **JK Flip-Flop**:

- Takes advantage of all combinations of two inputs (J & K) to produce four different behaviours:

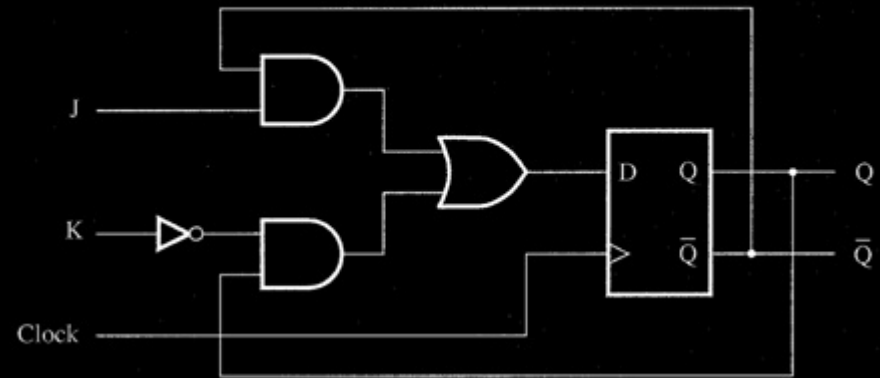- if J and K are 0, maintain output.
- if J is 0 and K is 1, set output to 0.
- if J is 1 and K is 0, set output to 1.
- if J and K are 1, toggle output value.



Sequential circuit design

- Similar to creating combinational circuits, with extra considerations:
 - The flip-flops now provide extra inputs to the circuit
 - Extra circuitry needs to be designed for the flip-flop inputs.
 - ...which is next 😊

