

Lecture 2 Review



Path Integrals over Complex Plane

- Let $f(z): \mathbb{C} \rightarrow \mathbb{R}$

- $\int_{z_1}^{z_2} f(z) dz = ?$



Lecture 2 Review

  - Question #1:
 - Express XOR using only NAND and NOT gates



Lecture 2 Review

  - Question #1b:
 - Implement XOR using only NAND gates
 - HINT: Implement NOT using NAND gates



Lecture 2 Review

- Question #2a:
 - Construct the truth table for the following requirement

When A is off, I want the output to be high whenever one of B or C are 1, but low when they're both 1 or both 0. When A is on, I want the output to be high when B and C are both 0 or both 1, and low otherwise.

A	B	C	Y
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Lecture 2 Review

- Question #2a:
 - Construct the truth table for the following requirement

When A is off, I want the output to be high whenever one of B or C are 1, but low when they're both 1 or both 0. When A is on, I want the output to be high when B and C are both 0 or both 1, and low otherwise.

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Lecture 2 Review

- Question #2b:
 - What are the minterms for the following table?
 - What is the SOM expression (non reduced)

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

$$Y = m_1 + m_2 + m_4 + m_7$$

$$Y = \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}B\bar{C} + ABC$$

Lecture 2 Review

- Question #3a
 - Complete the truth table

$$Y = m_0 + m_1 + m_2 + m_5 + m_7 + m_8 + m_9 + m_{10} + m_{13} + m_{15}$$

A	B	C	D	X
0	0	0	0	
0	0	0	1	
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	
0	1	1	0	
0	1	1	1	
1	0	0	0	
1	0	0	1	
1	0	1	0	
1	0	1	1	
1	1	0	0	
1	1	0	1	
1	1	1	0	
1	1	1	1	

Lecture 2 Review

- Question #3b
 - Construct the K-Map

	$\bar{C} \cdot \bar{D}$	$\bar{C} \cdot D$	$C \cdot D$	$C \cdot \bar{D}$
$\bar{A} \cdot \bar{B}$				
$\bar{A} \cdot B$				
$A \cdot B$				
$A \cdot \bar{B}$				

A	B	C	D	X
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1

Lecture 2 Review

- Question #3c:
 - Find the groupings and reduce the expression

	$\bar{C} \cdot \bar{D}$	$\bar{C} \cdot D$	$C \cdot D$	$C \cdot \bar{D}$
$\bar{A} \cdot \bar{B}$	1	1	0	1
$\bar{A} \cdot B$	0	1	1	0
$A \cdot B$	0	1	1	0
$A \cdot \bar{B}$	1	1	0	1

$$Y = BD + \bar{C}D + \bar{B}\bar{D}$$

Lecture 3

review

Question #1

- a) How do you write the number 78 as an 8-bit binary number?

128	64	32	16	8	4	2	1
0	1	0	0	1	1	1	0

- b) What is the two's complement of 01101101?

10010011

- c) What is 11001010 In decimal?

Unsigned

202

Signed (2's complement) -54

128	64	32	16	8	4	2	1
1	1	0	0	1	0	1	0

-128	64	32	16	8	4	2	1
1	1	0	0	1	0	1	0

Question #1

d) What is the sum of 01101101 and 01101101?

011011010

Don't forget to
add the extra 0
to the front

- Adding a number to itself \rightarrow multiply by 2
- Multiply by 2 \rightarrow shift bits to the left

Question #2


- What groupings are in the K-map on the right?

	$\bar{C} \cdot \bar{D}$	$C \cdot \bar{D}$	$C \cdot D$	$\bar{C} \cdot D$
$\bar{A} \cdot \bar{B}$	1	1	X	1
$A \cdot \bar{B}$	X	0	X	1
$A \cdot B$	1	X	X	1
$\bar{A} \cdot B$	1	X	0	X

- What logic equations do these groupings represent?

$$\bar{A} \cdot \bar{B} + \bar{C}$$

Question #3

 


- Implement a half adder in Verilog.
- **Step 1:** What is the half adder logic equation?

$$\begin{aligned} \mathbf{C} &= X \cdot Y & \mathbf{S} &= X \cdot \bar{Y} + \bar{X} \cdot Y \\ & & &= X \oplus Y \end{aligned}$$

- **Step 2:** Equivalent Verilog components.

```
assign C = X & Y;  
assign S = X & ~Y | ~X & Y;
```

Question #3 (cont'd)

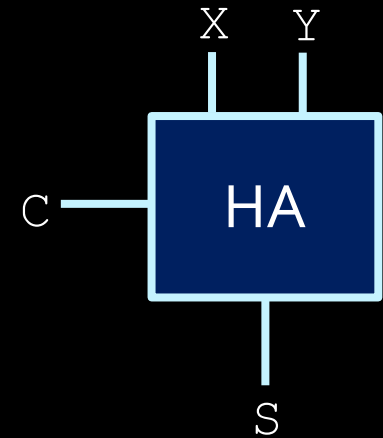

- **Step 3:** What is the complete Verilog code for this device?

```
module half_adder(X, Y, C, S);  
  input X, Y;  
  output C, S;  
  
  assign C = X & Y;  
  assign S = X & ~Y | ~X & Y;  
endmodule
```