

Lecture 4 Review

Question #1

- Find the groupings in the following K-Map

	$\bar{C} \cdot \bar{D}$	$\bar{C} \cdot D$	$C \cdot D$	$C \cdot \bar{D}$
$\bar{A} \cdot \bar{B}$	1	0	X	1
$\bar{A} \cdot B$	X	0	X	1
$A \cdot B$	1	X	1	1
$A \cdot \bar{B}$	1	X	X	X

- Produce a logical equation for these groupings:

$$A + \bar{D}$$

Question #1: alternative

- Find the groupings in the following K-Map


	$\bar{C} \cdot \bar{D}$	$\bar{C} \cdot D$	$C \cdot D$	$C \cdot \bar{D}$
$\bar{A} \cdot \bar{B}$	1	0	X	1
$\bar{A} \cdot B$	X	0	X	1
$A \cdot B$	1	X	1	1
$A \cdot \bar{B}$	1	X	X	X

- Produce a logical equation for these groupings:

$$\bar{D} + C$$

Question #2

- Complete the truth table

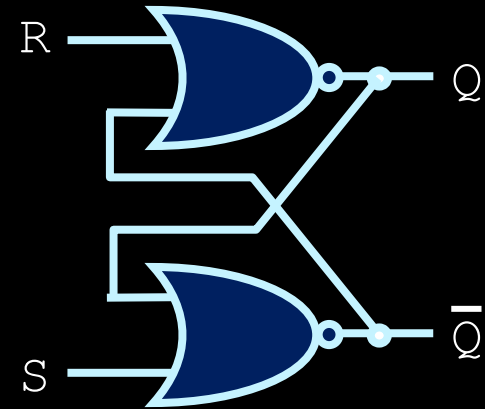

S	R	Q_T	\bar{Q}_T	Q_{T+1}	\bar{Q}_{T+1}

← Hold


← Reset

← Set

← Forbidden

Question #2


- Complete the truth table

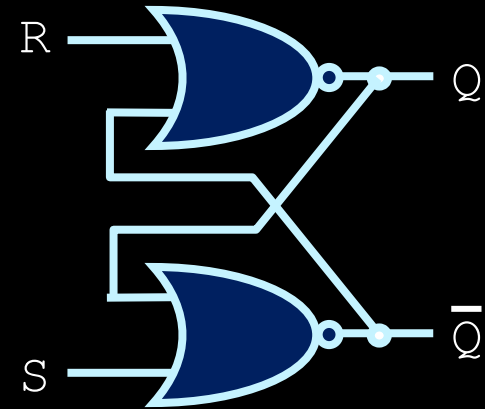

S	R	Q_T	\bar{Q}_T	Q_{T+1}	\bar{Q}_{T+1}	
0	0	0	1	0	1	← Hold
0	0	1	0	1	0	
0	1	X	X	0	1	← Reset
1	0	X	X	1	0	← Set
1	1	X	X	0	0	← Forbidden

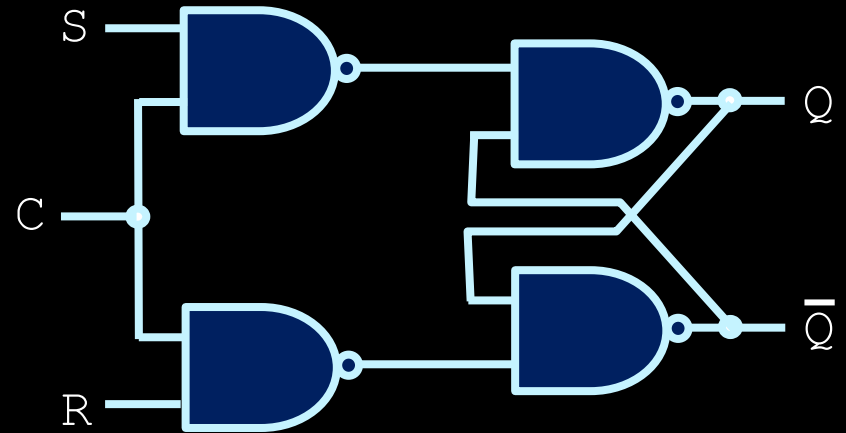Question #3

- What are the output values from Q and \bar{Q} given the following inputs on S , R and C ?




Time
↓

S	R	C	Q	\bar{Q}
0	0	1		
1	0	1		
1	0	0		
0	0	0		
0	1	0		
0	1	1		

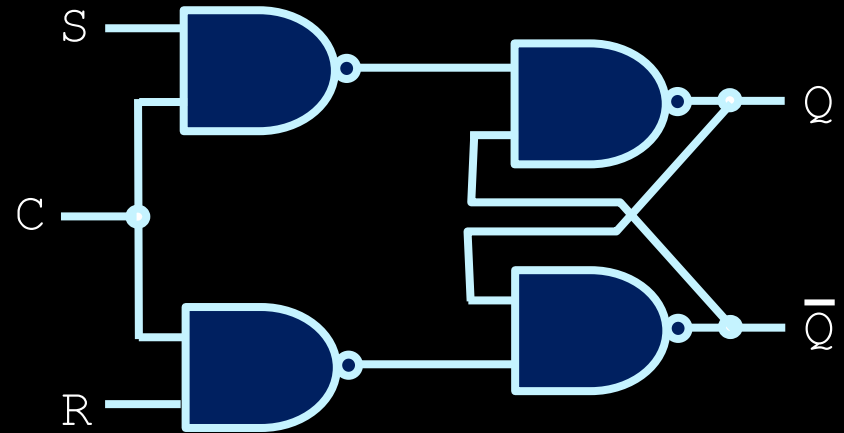Question #3

- What are the output values from Q and \bar{Q} given the following inputs on S , R and C ?





Time



S	R	C	Q	\bar{Q}
0	0	1	?	?
1	0	1	1	0
1	0	0	1	0
0	0	0	1	0
0	1	0	1	0
0	1	1	0	1

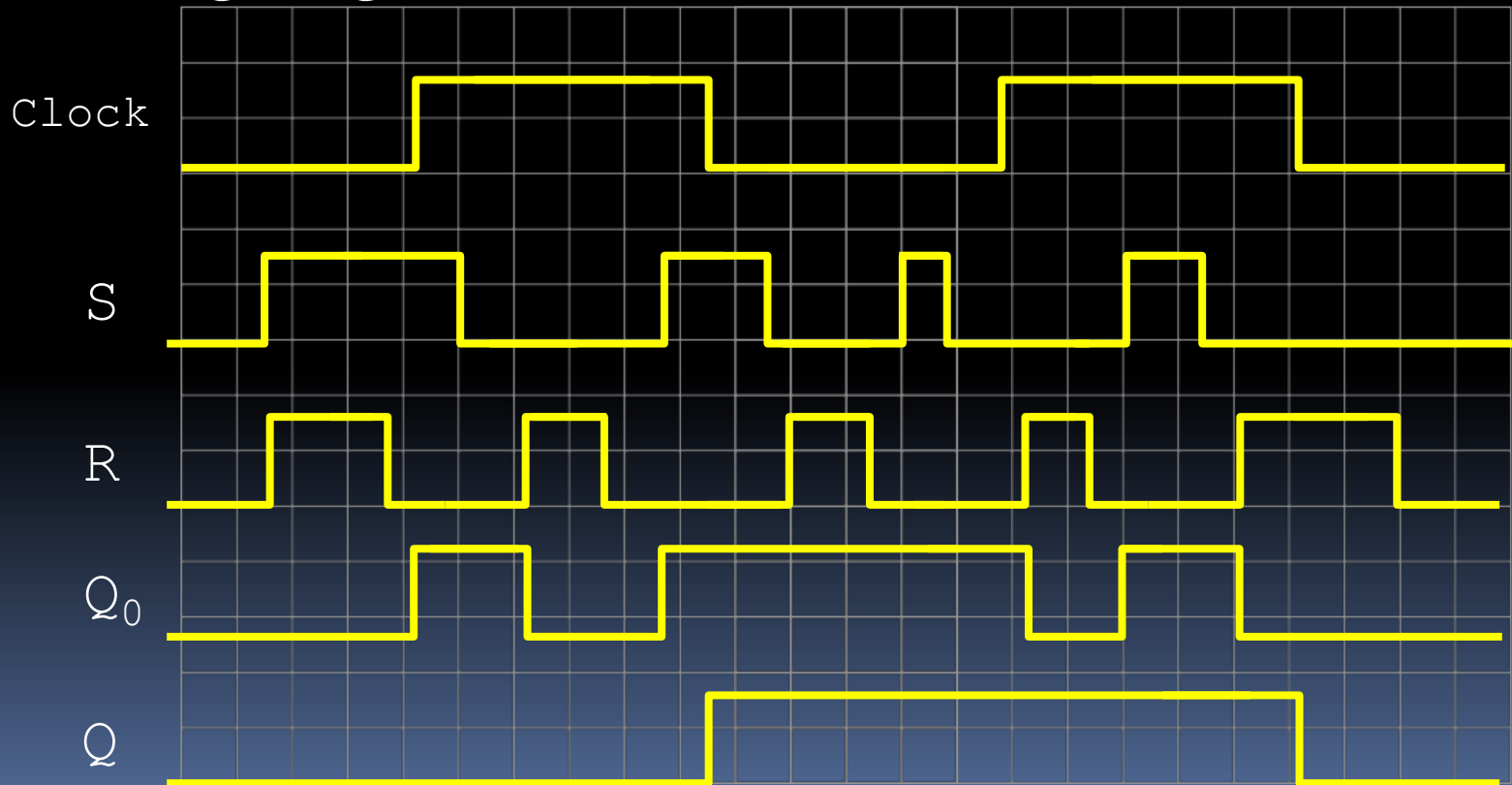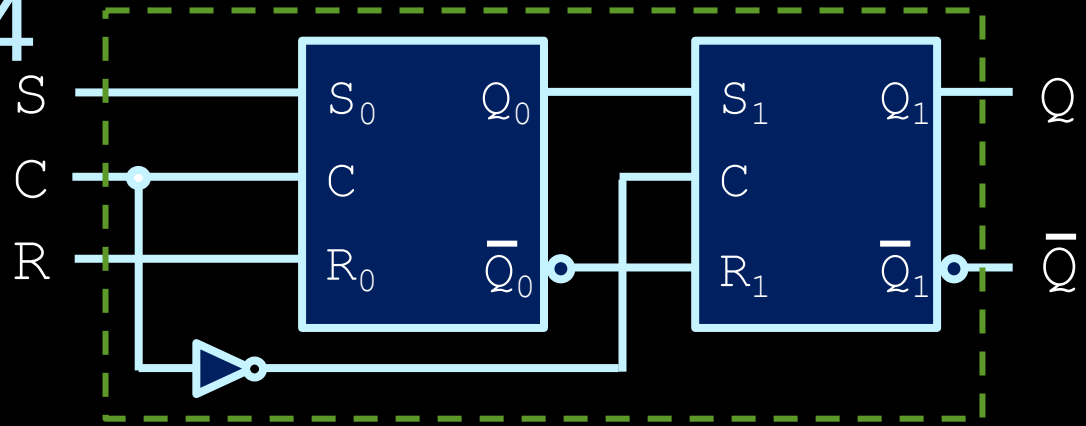Question #4

- Assuming all inputs start low, complete the timing diagram



Lecture 5 Review

Question #1

Assume we want to build a change machine

- We can add either **\$0.05** or **\$0.10** at a time
- We want to keep track of the current amount in the machine
- We can hold a **maximum of \$0.50**
- Draw the state diagram

Question #1b

- How many flip-flops would you need to implement the following finite state machine (FSM)?

- 11 states
- # flip-flops = $\lceil \log_2 (\# \text{ of states}) \rceil$
- # flip-flops = 4




Question 2: Barcode Reader

- When scanning UPC barcodes, the laser scanner looks for black and white bars that indicate the start of the code.
- If black is read as a 1 and white is read as a 0, the start of the code (from either direction) has a **1010 pattern**.
 - Can you create a state machine that detects this pattern?



Step #1: Draw state diagram

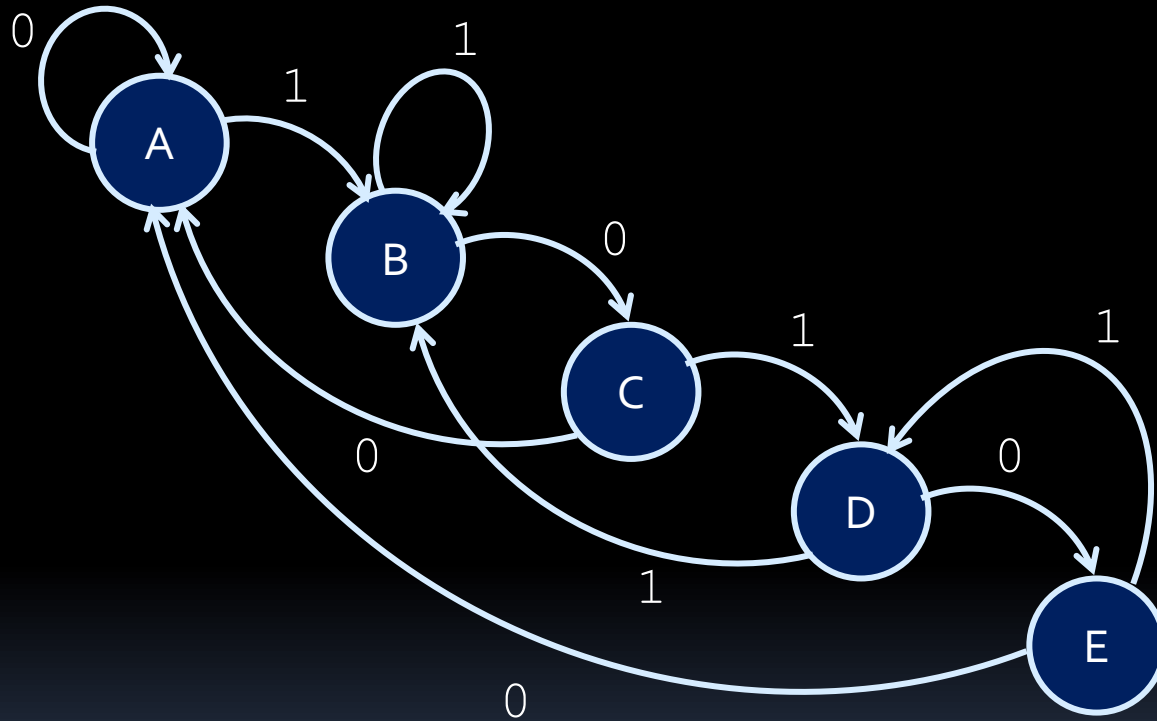

Step #2: State Table


- Write state table with Z
- Output Z is determined by the current state.
 - Denotes Moore machine.
- Next step: allocate flip-flops values to each state.
 - How many flip-flops will we need for 5 states?
 - # flip-flops = $\lceil \log(\# \text{ of states}) \rceil$

Present State	X	Z	Next State
A	0	0	A
A	1	0	B
B	0	0	C
B	1	0	B
C	0	0	A
C	1	0	D
D	0	0	E
D	1	0	B
E	0	1	A
E	1	1	D

Step #3: Flip-Flop Assignment

- 3 flip-flops needed here.
- Assign states carefully though!
- Can't simply do this:

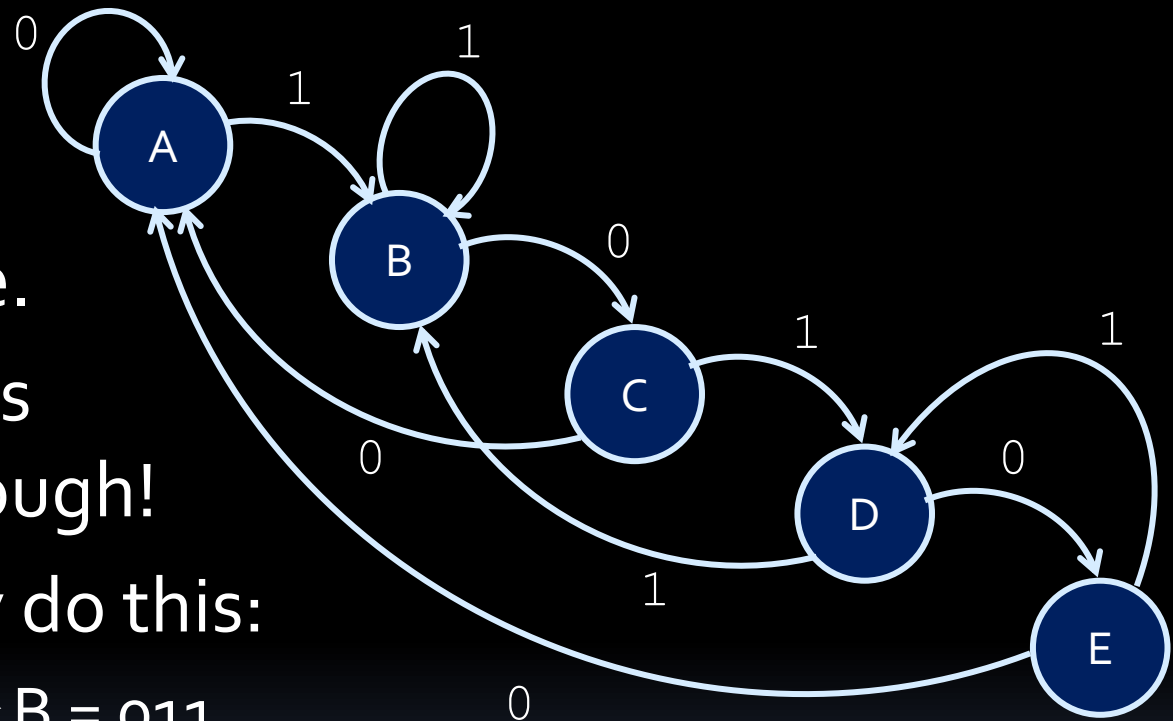- A = 100 ➤ B = 011
- C = 010 ➤ D = 001
- E = 000



Why not?

Step #3: Flip-Flop Assignment

- Be careful of **race conditions**.


- Better solution:

➤ A = 000 ➤ B = 001

➤ C = 011 ➤ D = 101

➤ E = 100

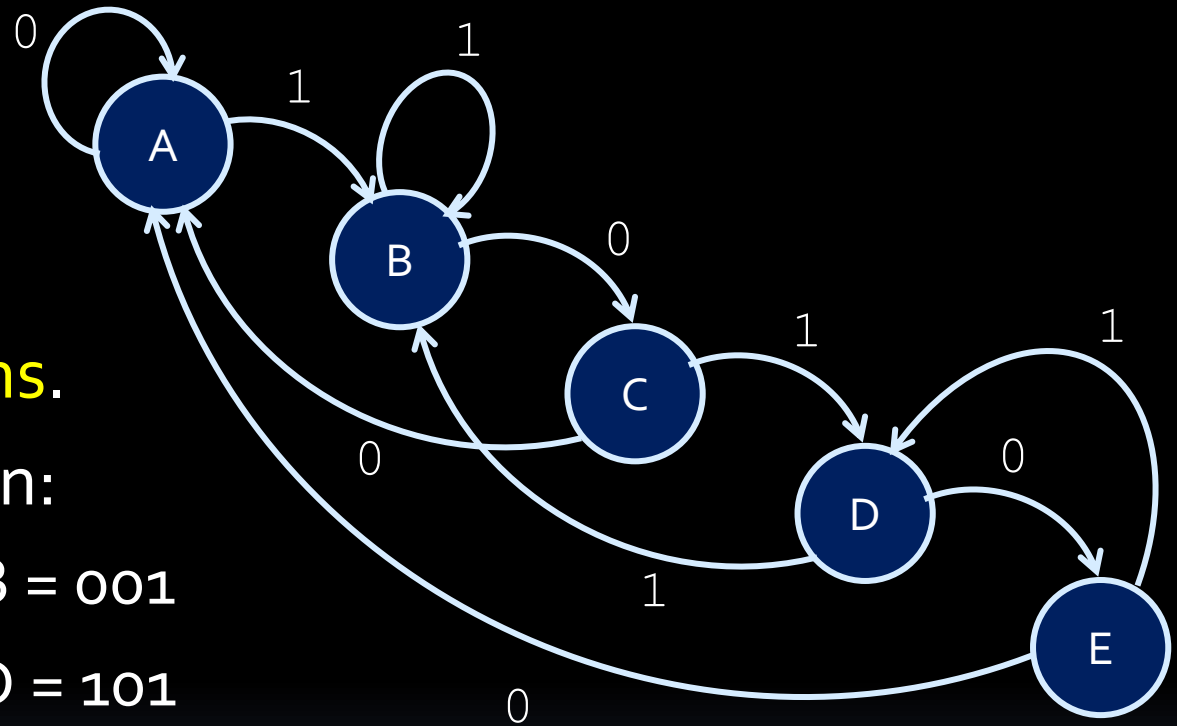- Still has race conditions ($C \rightarrow D$, $C \rightarrow A$), but is safer.
 - “Safer” is defined according to output behaviour.
 - Sometimes, extra flip-flops are used for extra insurance.



Step #4: Redraw State Table

- From here, we can construct the K-maps for the state logic combinational circuit.
 - Derive equations for each flip-flop value, given the previous values and the input X .
 - Three equations total, plus one more for Z (trivial for Moore machines).

F_2	F_1	F_0	X	Z	F_2	F_1	F_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	0	1
0	1	1	0	0	0	0	0
0	1	1	1	0	1	0	1
1	0	1	0	0	1	0	0
1	0	1	1	0	0	0	1
1	0	0	0	1	0	0	0
1	0	0	1	1	1	0	1

Step 5: Circuit design

- Karnaugh map for F_2 :

	$\overline{F_0} \cdot \overline{X}$	$\overline{F_0} \cdot X$	$F_0 \cdot X$	$F_0 \cdot \overline{X}$
$\overline{F_2} \cdot \overline{F_1}$	0	0	0	0
$\overline{F_2} \cdot F_1$	X	X	1	0
$F_2 \cdot F_1$	X	X	X	X
$F_2 \cdot \overline{F_1}$	0	1	0	1

$$F_2 = F_1X + F_2\overline{F_0}X + F_2F_0\overline{X}$$

Step 5: Circuit design

- Karnaugh map for F_1 :

	$\overline{F_0} \cdot \overline{X}$	$\overline{F_0} \cdot X$	$F_0 \cdot X$	$F_0 \cdot \overline{X}$
$\overline{F_2} \cdot \overline{F_1}$	0	0	0	1
$\overline{F_2} \cdot F_1$	X	X	0	0
$F_2 \cdot F_1$	X	X	X	X
$F_2 \cdot \overline{F_1}$	0	0	0	0

$$F_1 = \overline{F_2} \overline{F_1} F_0 \overline{X}$$

Step 5: Circuit design

- Karnaugh map for F_0 :

	$\overline{F_0} \cdot \overline{X}$	$\overline{F_0} \cdot X$	$F_0 \cdot X$	$F_0 \cdot \overline{X}$
$\overline{F_2} \cdot \overline{F_1}$	0	1	1	1
$\overline{F_2} \cdot F_1$	X	X	1	0
$F_2 \cdot F_1$	X	X	X	X
$F_2 \cdot \overline{F_1}$	0	1	1	0

$$F_0 = X + \overline{F_2} \overline{F_1} F_0$$

Step 5: Circuit design

- Output value Z goes high based on the following output equation:

$$Z = F_2 \overline{F_1} \overline{F_0}$$

- Note: All of these equations would be different, given different flip-flop assignments!
 - Practice alternate assignment for the midterm 😊